


Lab 05

Simple Vs Low Compliance Cascode Current Mirror

Part 1: Sizing Chart


- Given Parameters in this Lab:

MOSFET Length L	1um
Supply Voltage V_{ds}	1.8V
Drain Current I_D	20uA
Real MOSFET Overdrive Voltage V^*	0.2V

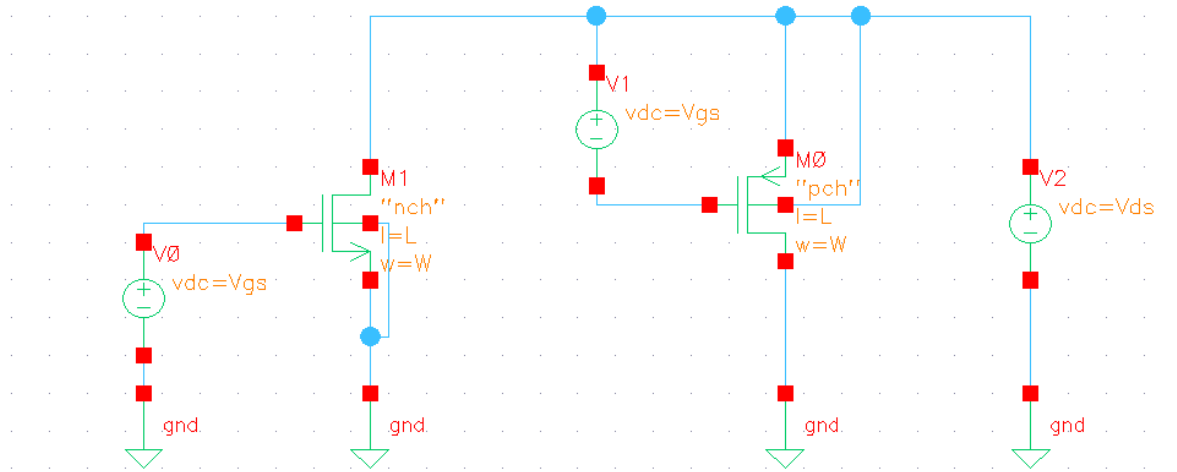


Schematic used in sizing

- Determine NMOS Width Value (W_n):

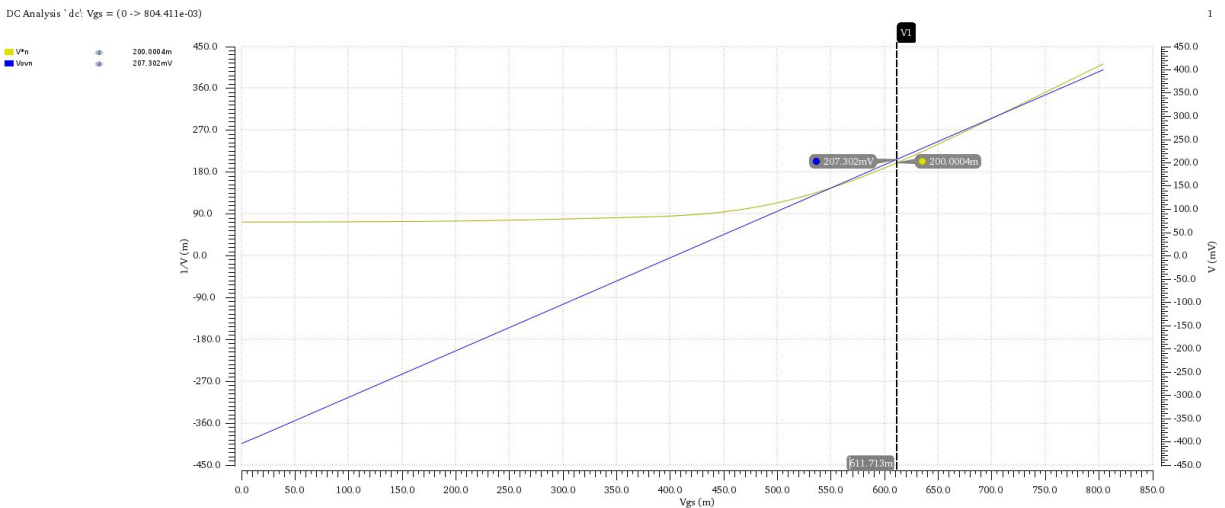

V_{ov} & V^* versus V_{gs} sweep

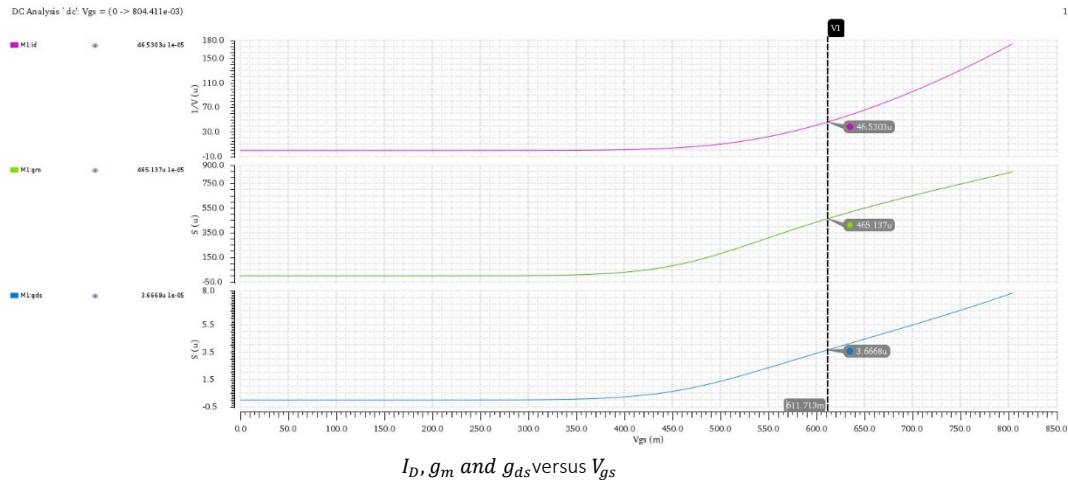From previous graphs we find at $V_Q^* = 200mV \rightarrow V_{gsQ} = 611.713mV$ and $V_{ovQ} = 207.3102mV$.




From previous graph at $V_{gs} = 611.713mV$, we have $I_{dX} = 46.5303uA$, $g_{mX} = 465.137uS$ and $g_{dsX} = 3.6668uS$.


Using cross multiplication as $I_d \propto W$, we find that $W=4.23um$.

Also $g_m = 196.7529uS$, and $g_{ds} = 1.551nS$ @ $W=4.23um$.

- Determine PMOS Width Value (W_p):

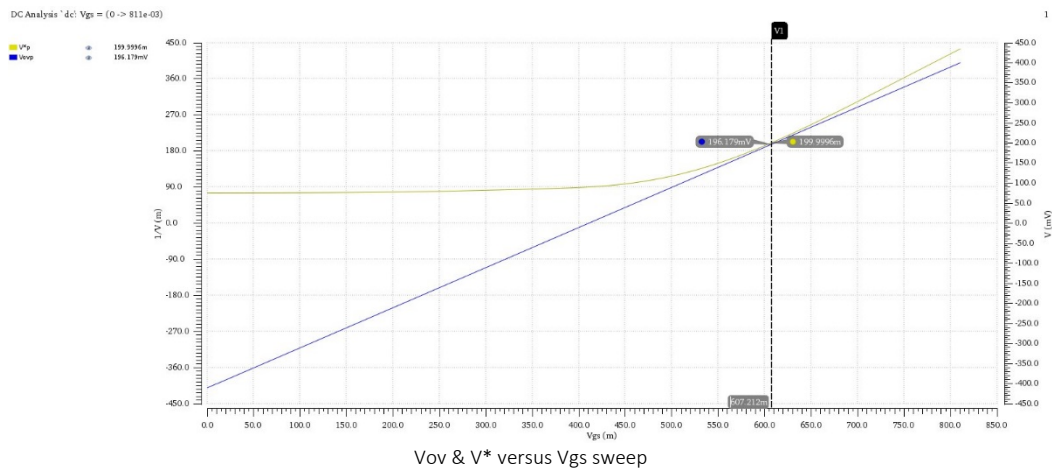

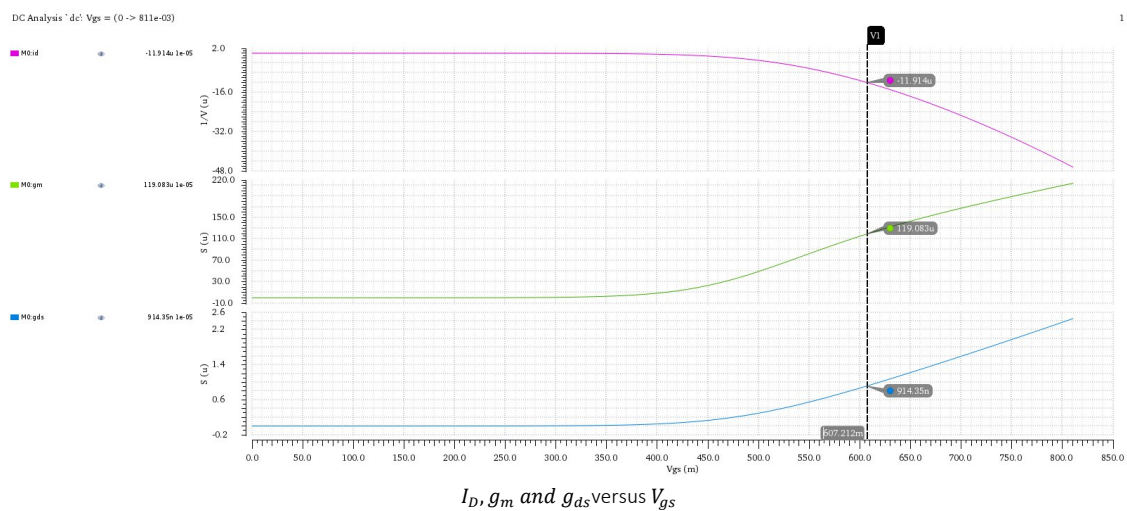From previous graphs we find at $V_Q^* = 200mV \rightarrow V_{gsQ} = 607.2124mV$ and $V_{ovQ} = 196.18mV$.




From previous graph at $V_{gs} = 607.2124mV$, we have $I_{dX} = 11.914uA$, $g_{mX} = 119.083uS$ and $g_{dsX} = 914.35nS$.


Using cross multiplication as $I_d \propto W$, we find that $W=16.787um$.

Also $g_m = 200uS$, and $g_{ds} = 1.535uS$ @ $W=16.787um$.


Part 2: Current Mirror

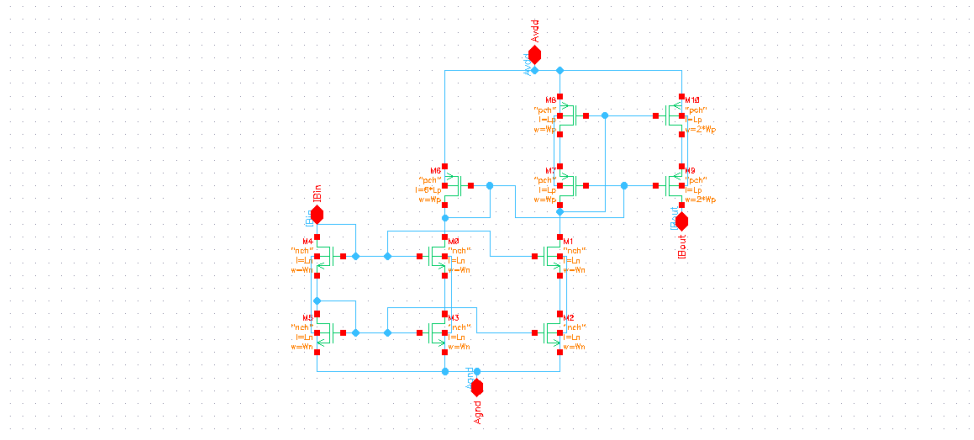

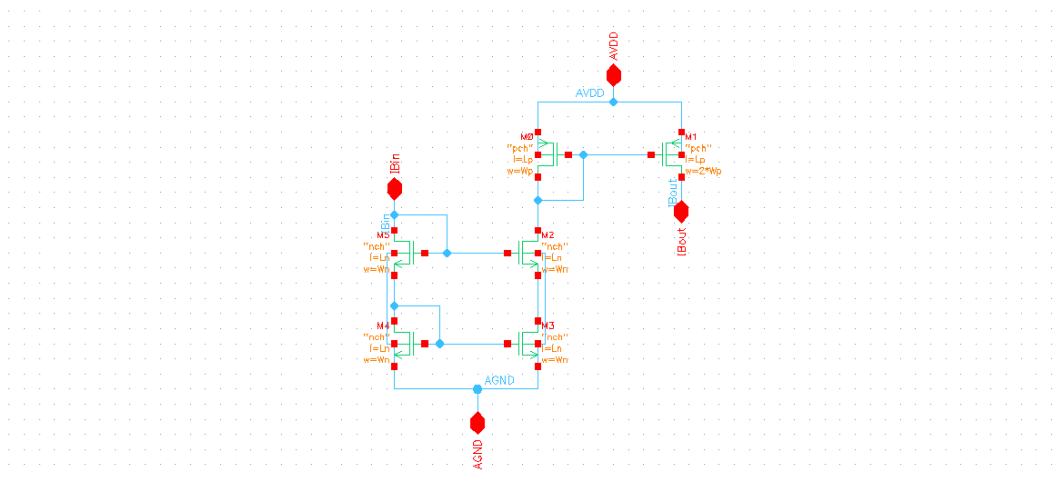
Wide sense current mirror schematic on cadence



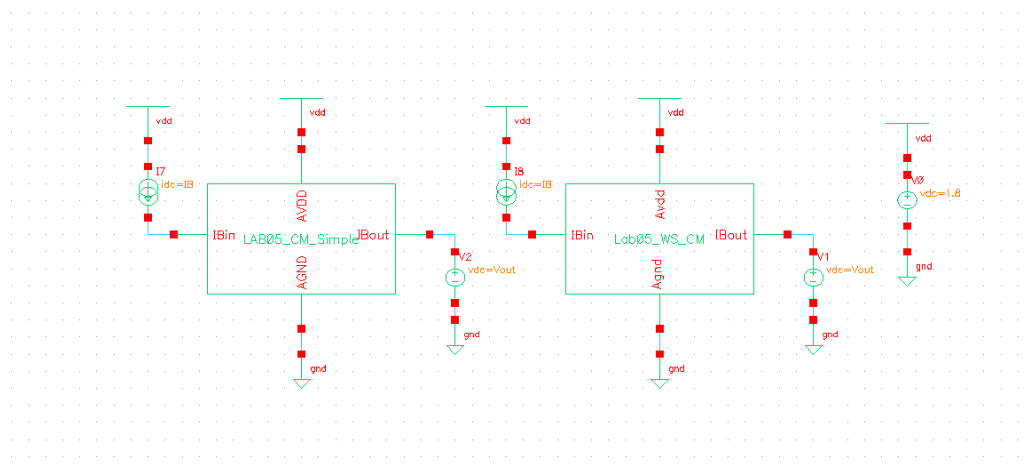
Simple cascode current mirror schematic on cadence



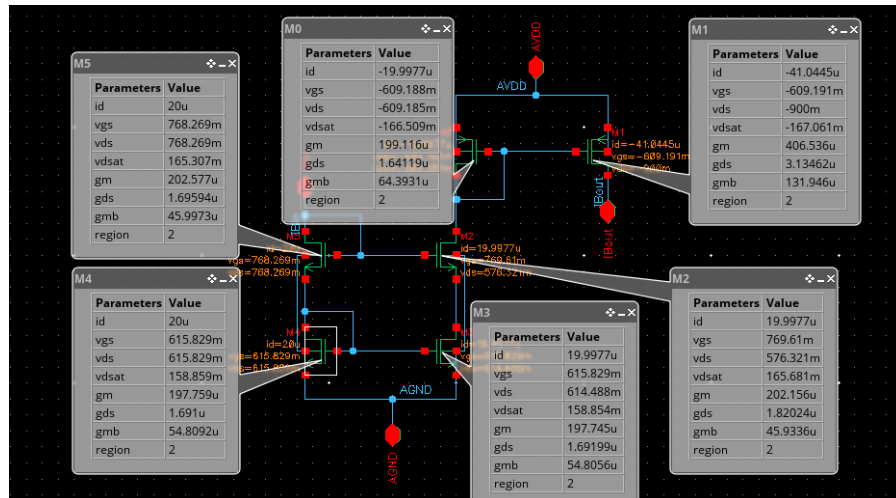WS & simple current mirrors symbols for testbench




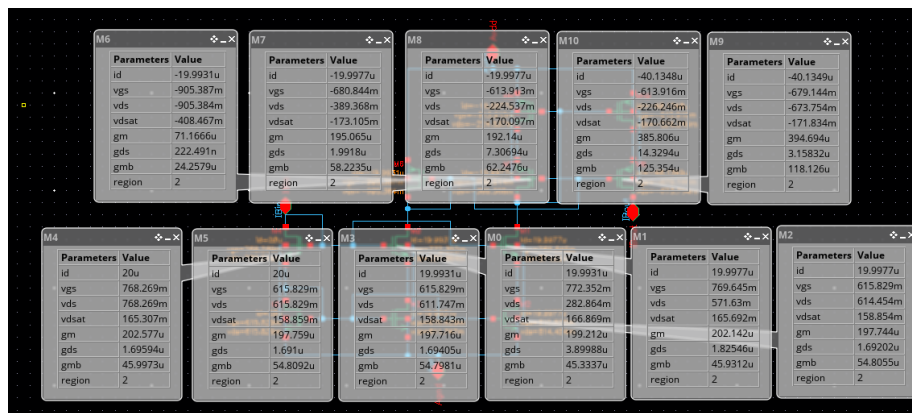Simple cascode current mirror Mosfets OP parameters




Wide sense cascode current mirror MOSFETs OP parameters

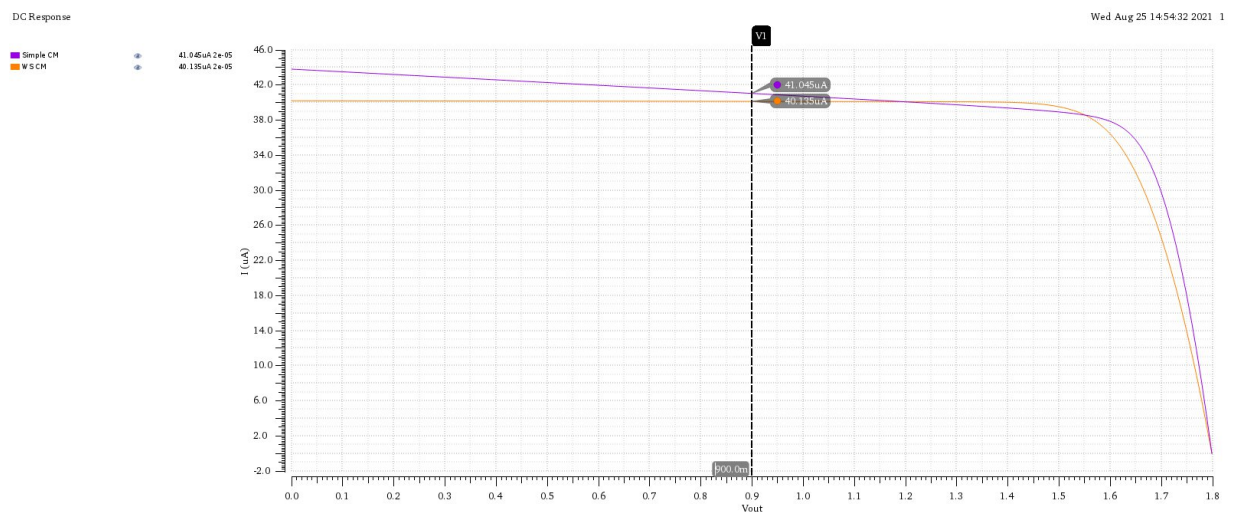- As shown in previous figures that all MOSFETs region equal 2 which mean that it operates in saturation region.
- From OP parameters shown in previous figures it's clear that results of Vgs, gm and gds are nearly to values calculated in part1.



output current versus Vout sweep for WS & simple current mirrors

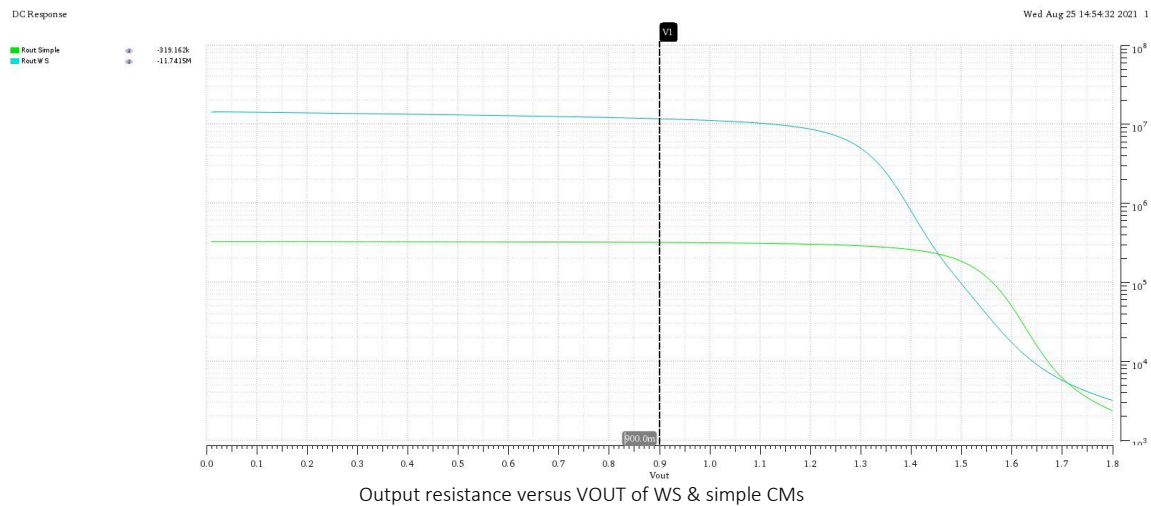- As shown from previous analysis that wide sense current mirror is more stable (constant current value) with voltage variations despite simple current mirror which changed with V_{out} variations.
- Because at this certain point voltage difference between V_{dd} and V_{out} provides the same V_{ds} to MOSFET as V_{DS} of magic battery which give perfect mirroring.



- Rout of wide sense CM is more than that of simple CM because output of wide sense CM is cascaded which give high impedance while simple CM is only a single transistor so its output impedance not boosted.
- No, Rout doesn't changed with V_{OUT} given that MOSFET operates in saturation, and Rout in this case is function in channel length which is constant value.

→ Simple CM @

$$(M_1) R_{out} = r_{o1} = \frac{1}{g_{ds1}} = \frac{1}{3.134} = 319.08 \text{ k}\Omega$$

" for Mosfet M1 in schematic "

→ wide sense CM @ (M_9 / M_{10})

$$R_{out} = r_{o9} (1 + (g_{m9} + g_{mb9}) r_{o10}) = \frac{g_{m9} + g_{mb9}}{g_{ds9} g_{ds10}}$$

$$R_{out} = 11.33 \text{ M}\Omega$$

Analytical calculations for Rout simple & WS CMs