

# Lab 04


## Common Drain Frequency Response

### Part 1: Sizing Chart


- Given Parameters in this Lab:

MOSFET Length L	1um
Supply Voltage $V_{ds}$	1.8V
Drain Current $I_D$	10uA
Real MOSFET Overdrive Voltage $V^*$	0.2V

- Determine PMOS Width Value (W):

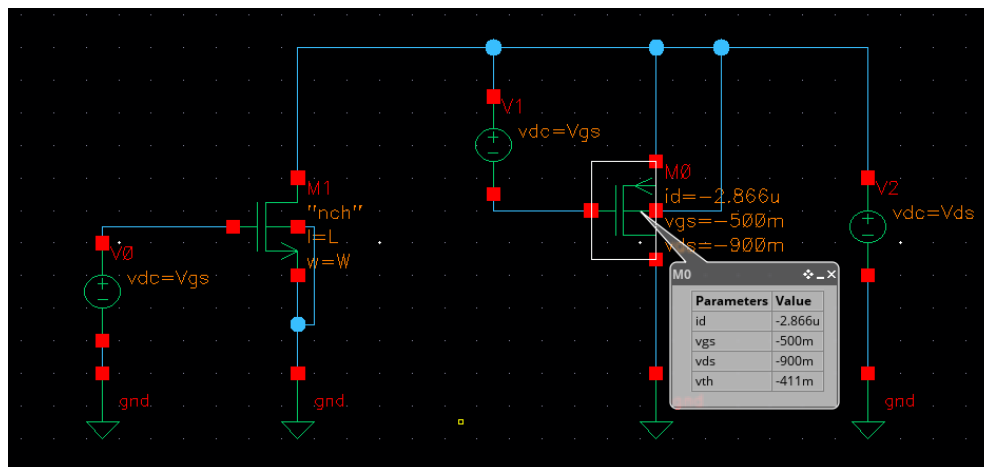


Design used for determine PMOS width

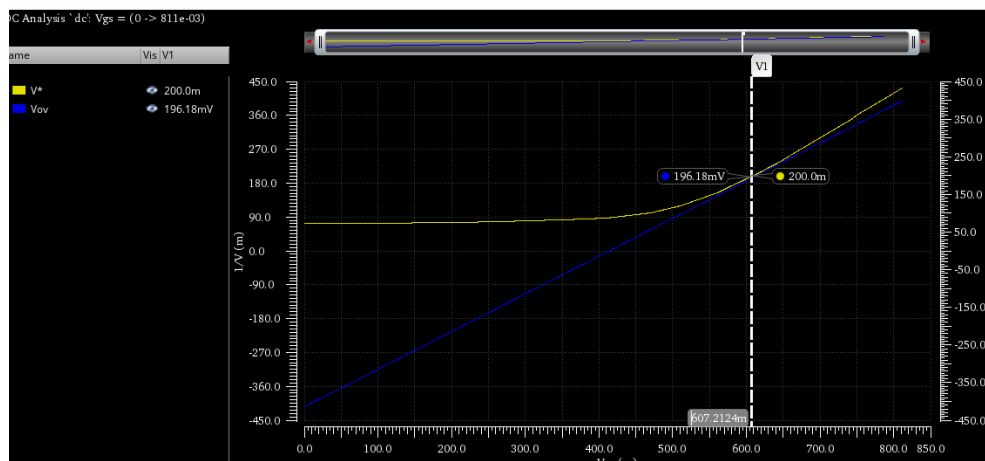

$V_{ov}$  &  $V^*$  versus  $V_{gs}$  sweep

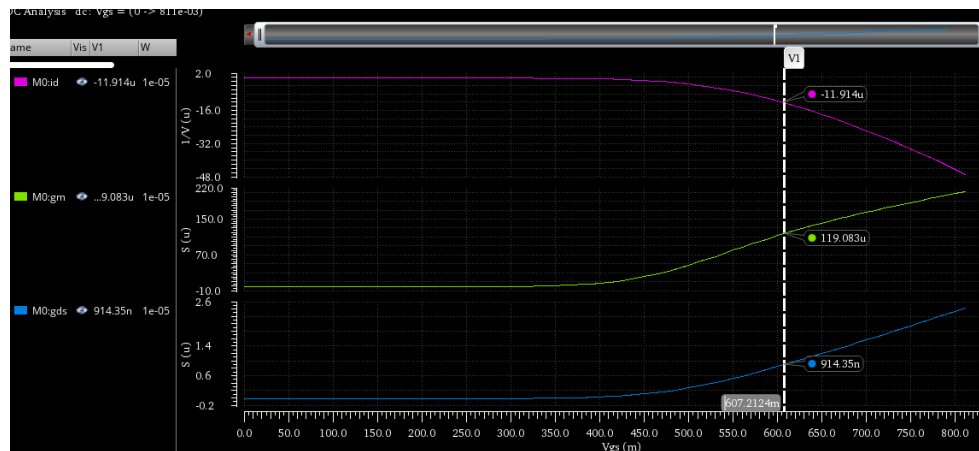From previous graphs we find at  $V_Q^* = 200mV \rightarrow V_{gsQ} = 607.2124mV$  and  $V_{ovQ} = 196.18mV$ .




From previous graph at  $V_{gs} = 607.2124\text{mV}$ , we have  $I_{dX} = 11.914\mu\text{A}$ ,  $g_{mX} = 119.083\mu\text{S}$  and  $g_{dsX} = 914.35\text{nS}$ .

Using cross multiplication as  $I_d \propto W$ , we find that  $W = 8.39\mu\text{m}$ .


Also  $g_m = 100\mu\text{S}$ , and  $g_{ds} = 767.14\text{nS}$  @  $W = 8.39\mu\text{m}$ .

## Part 2: CD Amplifier

### 1. OP Analysis:

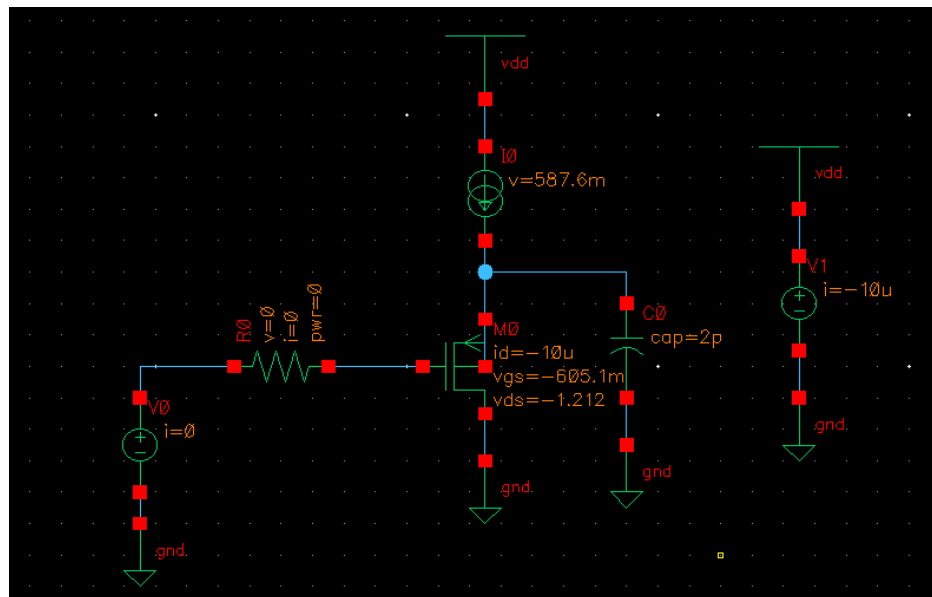

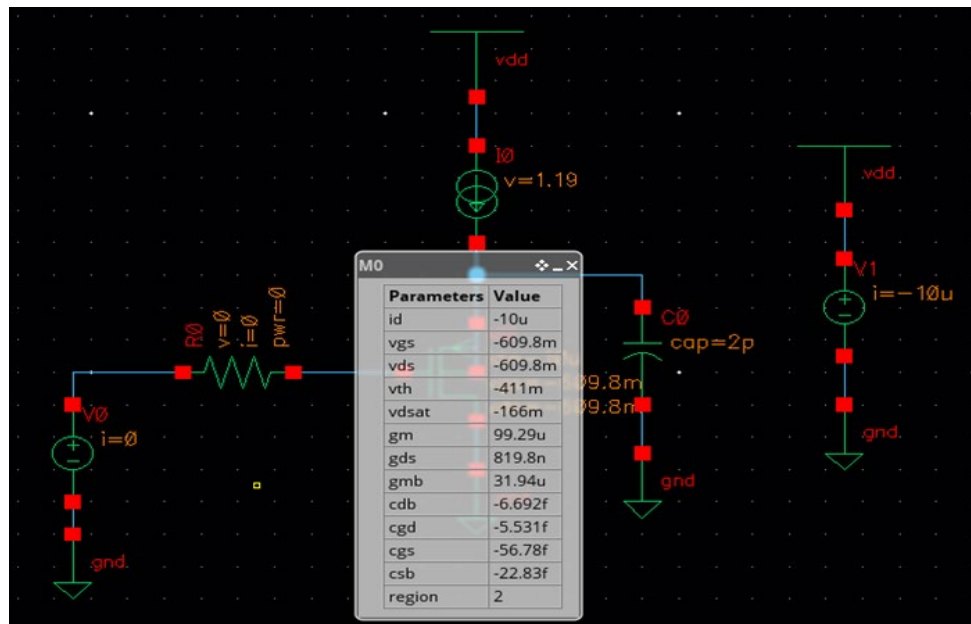
Circuit schematic for common drain amplifier



OP parameters for PMOS used in CD

- As shown region =2 so it operates in saturation

## 2. AC Analysis:

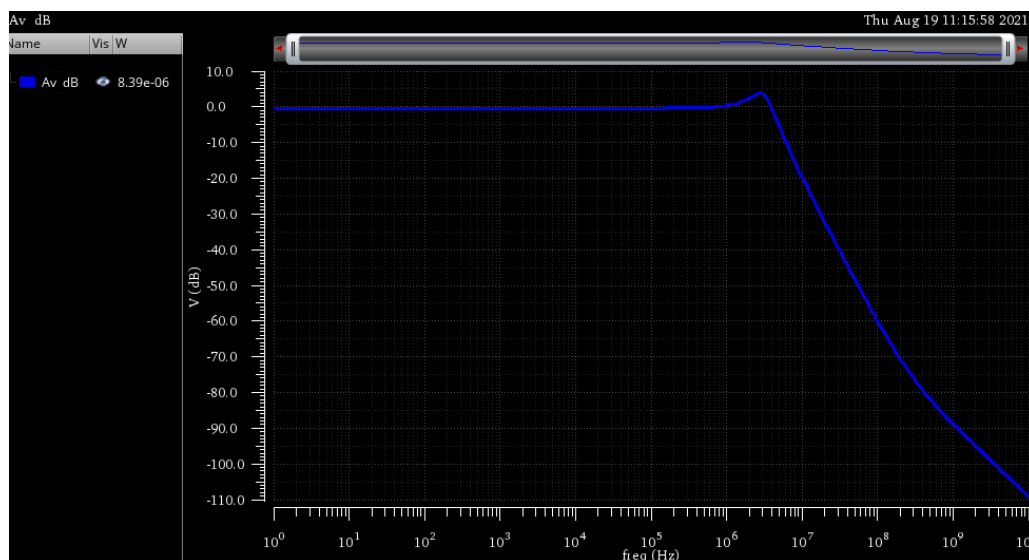

Bode plot magnitude for CD gain


- As shown from previous figure that there is a peaking in frequency domain which equals 4.288 dB.
- Quality Factor Calculations:

$Q = \frac{\sqrt{g_m(C_{gs} + C_{gd})R_{sig}}}{C_L} = 2.487$ , and hence  $Q > 0.707$  so system is underdamped system which proves peaking happens in frequency domain.


- Parametric Sweep for  $C_L$ :

Point	Test	Output	Nominal	Spec	Weight	Pass/Fail
Parameters: CL=2p						
1	TrainLAB:CD_Lab4:1	Av dB				
1	TrainLAB:CD_Lab4:1	Peaking	4.288			
Parameters: CL=4p						
2	TrainLAB:CD_Lab4:1	Av dB				
2	TrainLAB:CD_Lab4:1	Peaking	3.237			
Parameters: CL=8p						
3	TrainLAB:CD_Lab4:1	Av dB				
3	TrainLAB:CD_Lab4:1	Peaking	1.753			

CL parametric sweep results for CD

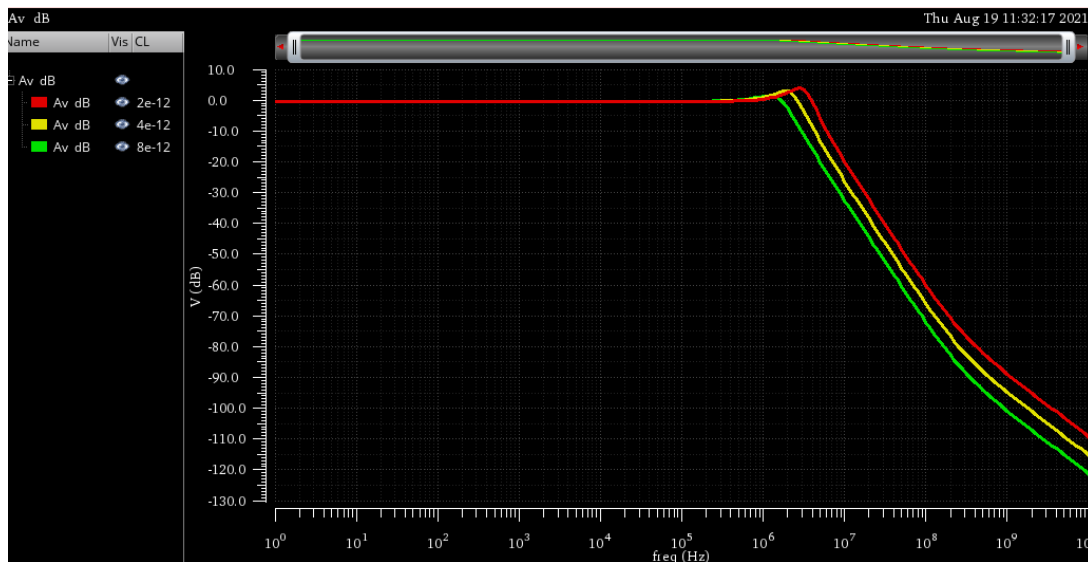

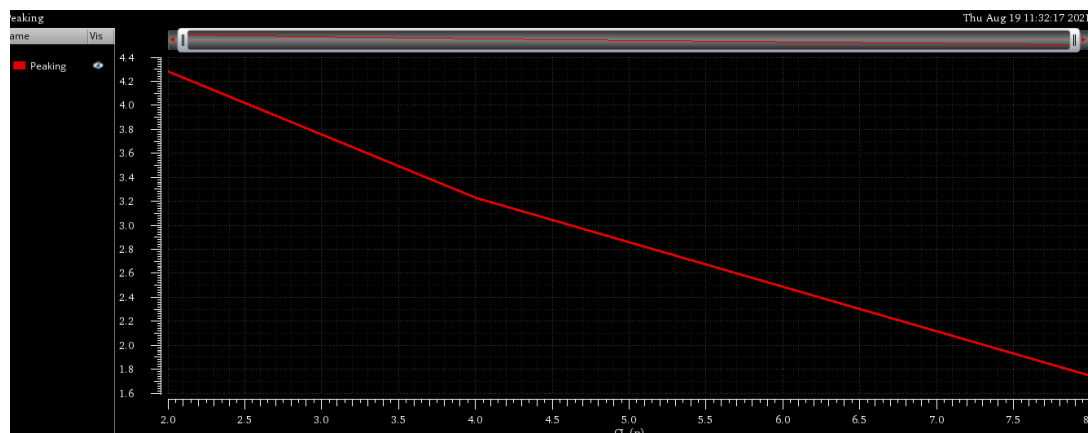Bode plot magnitude of gain after sweep load capacitance CL





Peaking versus load capacitance CL

Comment:

From previous results as shown that by increasing CL peaking decrease because that quality factor decreases also so it doesn't become underdamped anymore.

- Parametric Sweep for  $R_{sig}$ :

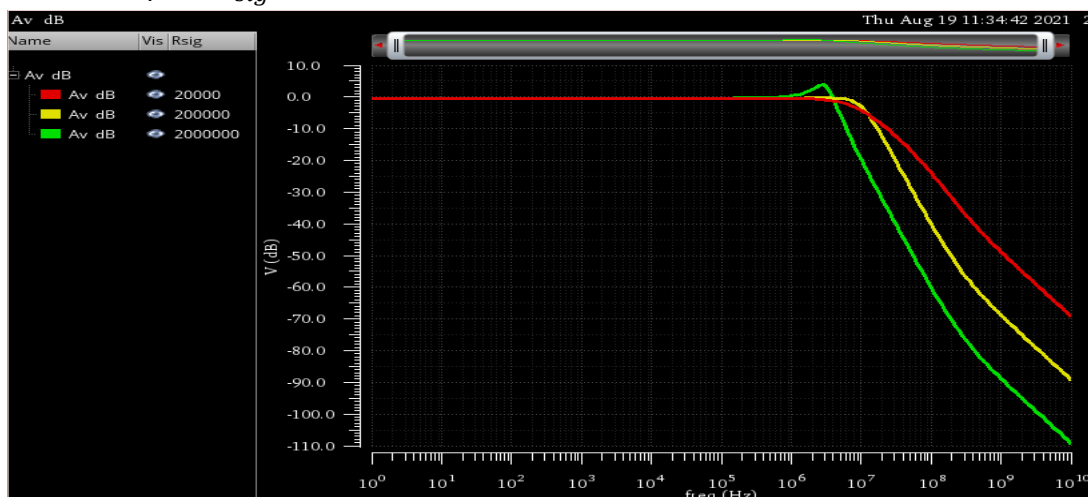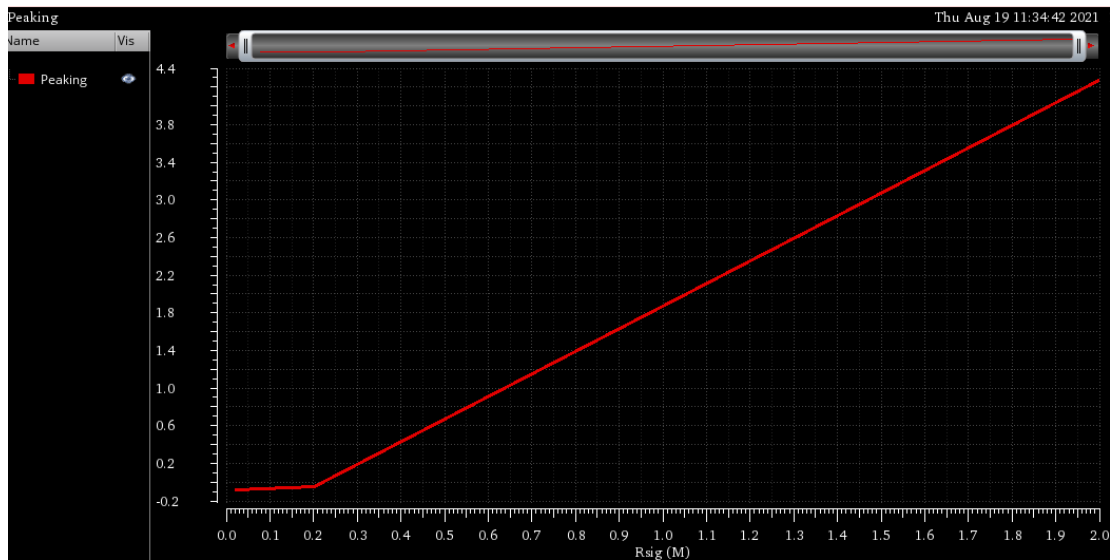Bode plot magnitude of gain after sweep  $R_{sig}$




Peaking versus Rsig

Comment:

As shown that by increasing Rsig quality factor increases and also peaking increases.

### 3. Transient Analysis:

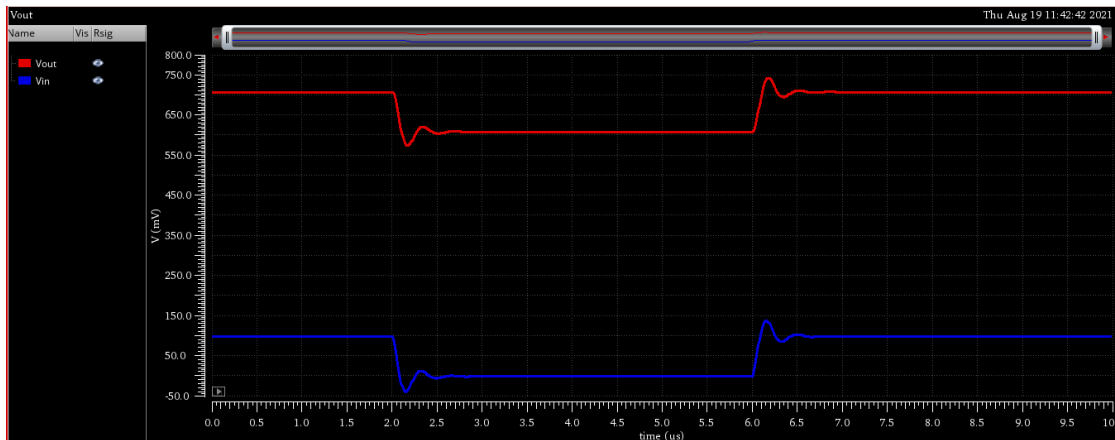

Vin &amp; Vout versus time

- DC Shift between Vout&Vin:
  - 1) DC shift between Vin and Vout equals  $V_{gs}$  because common drain amplifier considered as voltage buffer (source follower), so it doesn't affect on gain but only shift DC level for input signal.
  - 2) If we want to shift signal down use NMOS common drain stage.
- As shown from previous figure that there is ringing in time domain because our system is underdamped system as have been proved in previous part from quality factor calculations.
- Overshoot equals from cadence 34.83%


Parameters: CL=2p					
1	TrainLAB:CD_Lab4:1	Vout			
1	TrainLAB:CD_Lab4:1	Vin			
1	TrainLAB:CD_Lab4:1	Overshoot		34.83	

Overshoot results from ADXL cadence

- Parametric Sweep for CL:



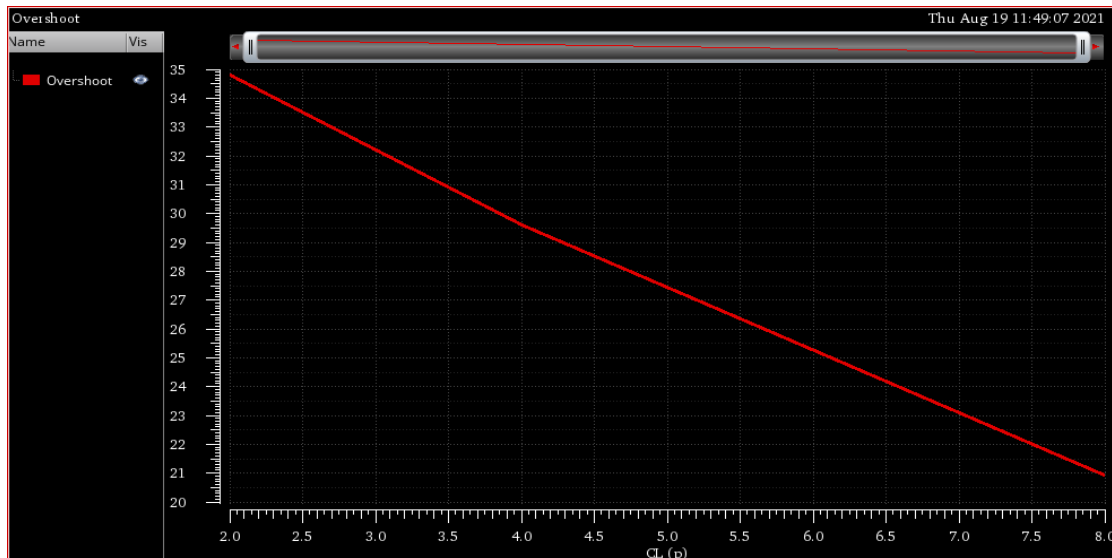Vout & Vin versus time after CL parametric sweep



Overshoot versus CL sweep


Comment:

From previous results as shown that by increasing CL overshoot decrease because that quality factor decreases also so it doesn't become underdamped anymore.

- Parametric Sweep for  $R_{sig}$ :



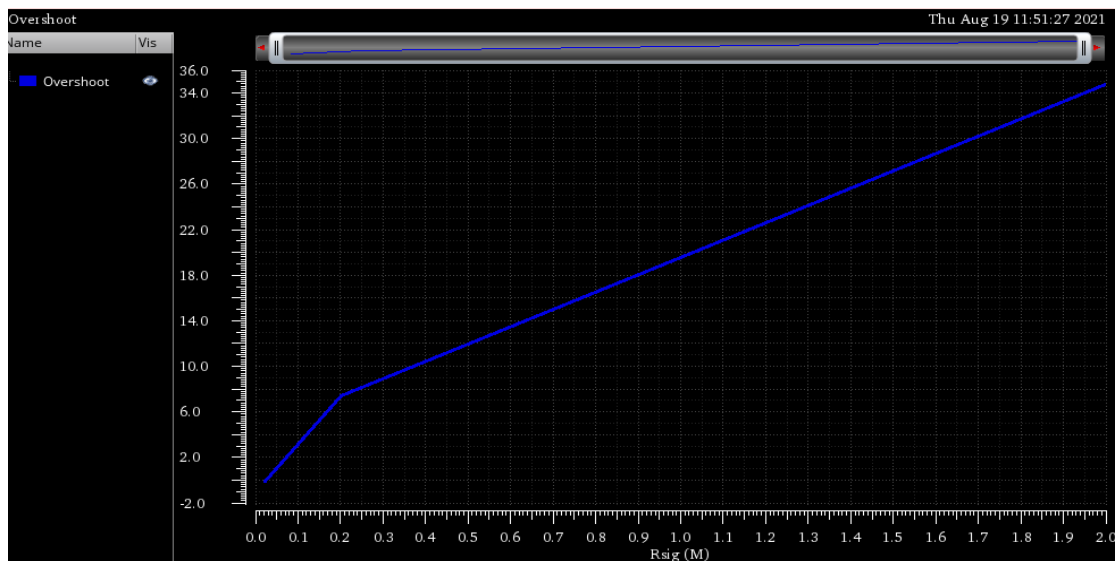$V_{out}$  &  $V_{in}$  versus time after  $R_{sig}$  parametric sweep




Overshoot versus CL sweep


Comment:

As shown that by increasing  $R_{sig}$  quality factor increases and also overshoot increases.

#### 4. $Z_{out}$ (Inductive Rise):

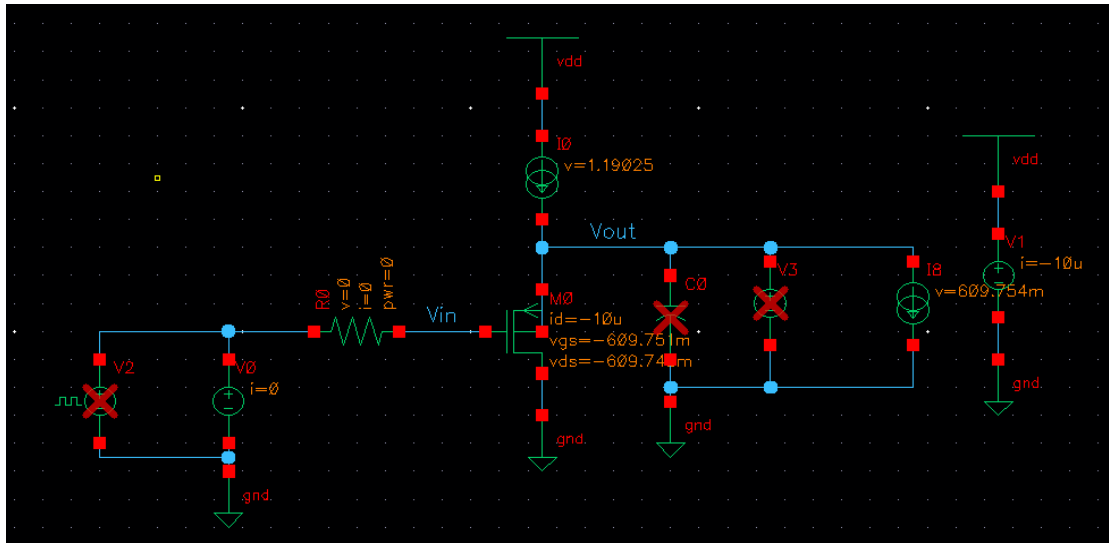

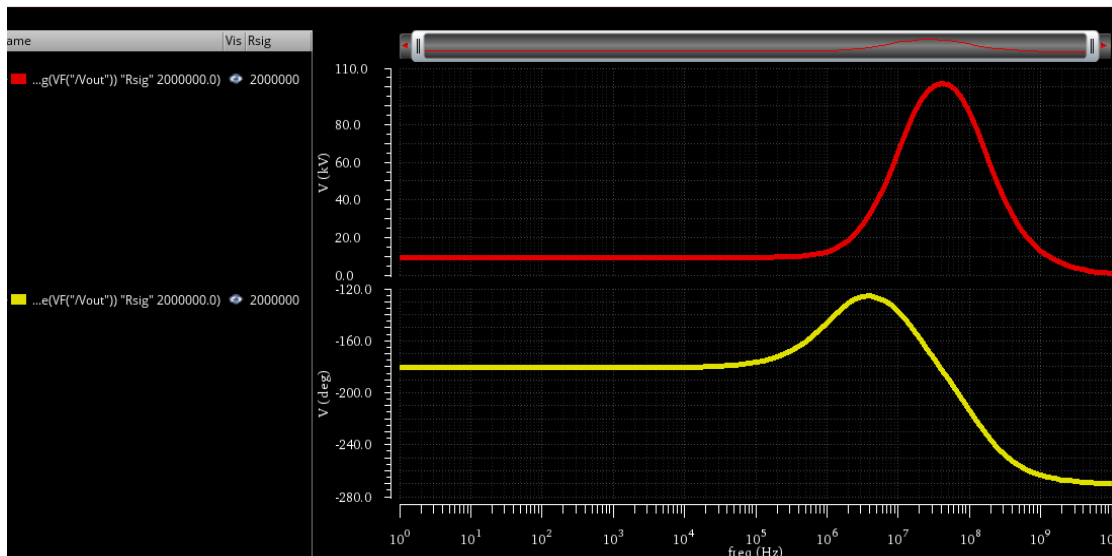Circuit schematic for  $Z_{out}$  calculations




$Z_{out}$  magnitude and phase versus frequency

- From previous analysis there is an inductive rise in output impedance because  $R_{sig}$  get into action at certain frequency and become greater than  $1/g_m$ .
- Yes, output impedance falls at high frequency as shown because of  $C_{gd}$  which become effective at high frequencies.



- Pole Zero Analysis:

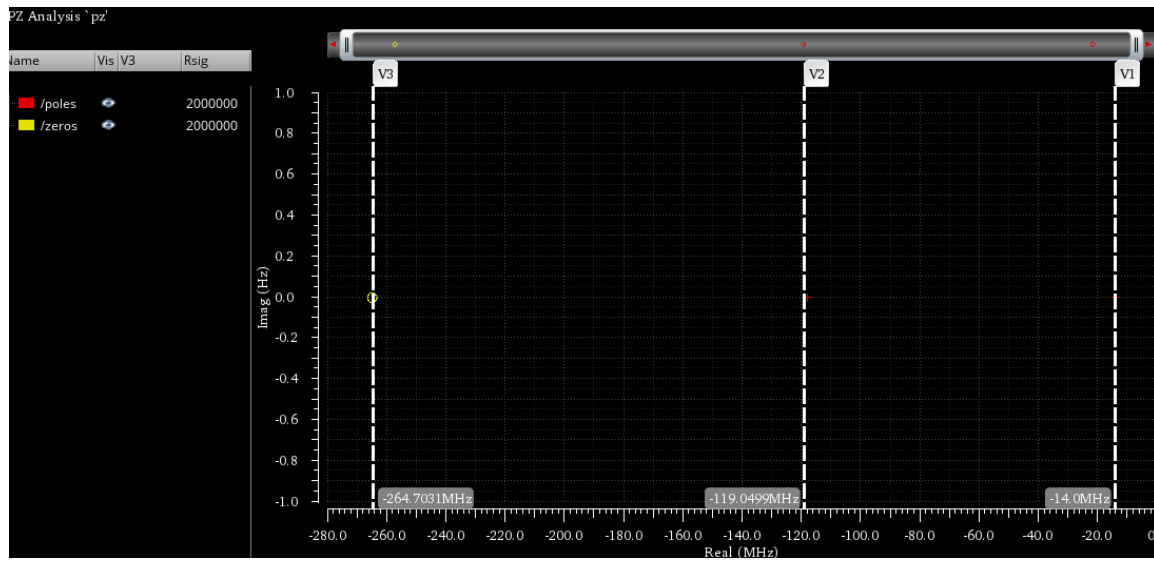

s-plan for pole zero analysis Zout results