



Analog IC Design

Labs Simulations & Results



Lab 01

LPF Simulations and MOSFET Characteristics

Part 1: Low Pass Filter Simulation (LPF)

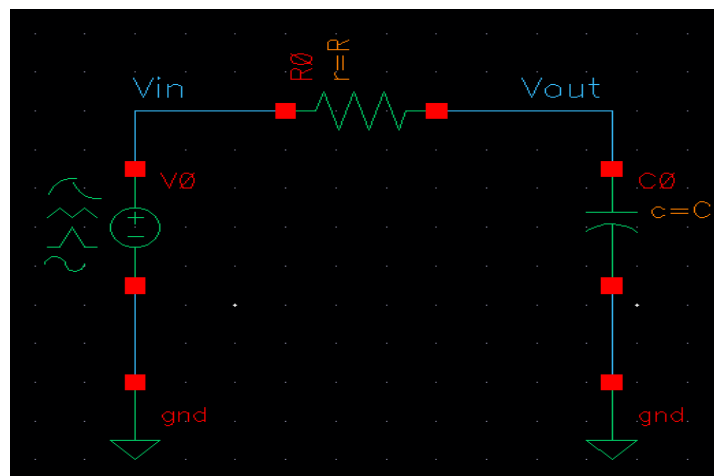


Fig.1 circuit schematic

1. Transient Analysis:

 


Fig.2 transient analysis with 2 CLK periods

$R=1\text{ k}\Omega$, $C=1\text{ pF}$, $\tau=1\text{ ns}$.

The analytical results of fall time and rise time calculations are evaluated by the following relation: **$T_R = T_F =$**

$2.2RC \approx 2.2\text{ ns}$.

Comment: on high values of R LPF begin to act as integrator as shown in the following figure.



Test	Output	Nominal	Spec	Weight	Pass/Fail
Analog_IC_Design_Course:LPF_Simulation:1	/Vout				
Analog_IC_Design_Course:LPF_Simulation:1	/Vin				
Analog_IC_Design_Course:LPF_Simulation:1	rise time	2.196n			
Analog_IC_Design_Course:LPF_Simulation:1	fall time	2.189n			

Fig.3 rise time and fall time calculations

 


Fig.4 parametric sweep for different values of R








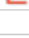


Point	Test	Output	Nominal	Spec	Weight	Pass/Fail
Parameters: R=1k						
1	Analog_IC_Design_Course:LPF_Simulation:1	/Vout				
1	Analog_IC_Design_Course:LPF_Simulation:1	/Vin				
1	Analog_IC_Design_Course:LPF_Simulation:1	rise time	2.196n			
1	Analog_IC_Design_Course:LPF_Simulation:1	fall time	2.189n			
Parameters: R=2k						
2	Analog_IC_Design_Course:LPF_Simulation:1	/Vout				
2	Analog_IC_Design_Course:LPF_Simulation:1	/Vin				
2	Analog_IC_Design_Course:LPF_Simulation:1	rise time	4.387n			
2	Analog_IC_Design_Course:LPF_Simulation:1	fall time	4.39n			
Parameters: R=3k						
3	Analog_IC_Design_Course:LPF_Simulation:1	/Vout				
3	Analog_IC_Design_Course:LPF_Simulation:1	/Vin				
3	Analog_IC_Design_Course:LPF_Simulation:1	rise time	6.582n			
3	Analog_IC_Design_Course:LPF_Simulation:1	fall time	6.562n			
Parameters: R=4k						
4	Analog_IC_Design_Course:LPF_Simulation:1	/Vout				
4	Analog_IC_Design_Course:LPF_Simulation:1	/Vin				
4	Analog_IC_Design_Course:LPF_Simulation:1	rise time	8.769n			
4	Analog_IC_Design_Course:LPF_Simulation:1	fall time	8.787n			
Parameters: R=5k						
5	Analog_IC_Design_Course:LPF_Simulation:1	/Vout				
5	Analog_IC_Design_Course:LPF_Simulation:1	/Vin				

Fig.5 different results of rise time and fall time after parametric sweep

2. AC Analysis:

 


Fig.6 bode plot of LPF circuit simulation

Comment: as the resistance value increase time constant τ increase and the cut off frequency decreases and also the bandwidth and this shown in the following figure from parametric sweep simulation. $w_c = \frac{1}{\tau} = \frac{1}{RC}$

Test	Output	Nominal	Spec	Weight	Pass/Fail
Analog_IC_Design_Course:LPF_Simulation:1	/Vout				
Analog_IC_Design_Course:LPF_Simulation:1	gain	1			
Analog_IC_Design_Course:LPF_Simulation:1	bandwidth	158.8M			
Analog_IC_Design_Course:LPF_Simulation:1	dc gain	0			
Analog_IC_Design_Course:LPF_Simulation:1	phase(VF("/Vout"))				

Fig.7 bandwidth and gain calculations from LPF


 


Fig.8 parametric sweep AC analysis

Point	Test	Output	Nominal	Spec	Weight	Pass/Fail
Parameters: R=1k						
1	Analog_IC_Design_Course:LPF_Simulation:1	mag plot				
1	Analog_IC_Design_Course:LPF_Simulation:1	bandwidth	158.8M			
Parameters: R=10k						
2	Analog_IC_Design_Course:LPF_Simulation:1	mag plot				
2	Analog_IC_Design_Course:LPF_Simulation:1	bandwidth	15.88M			
Parameters: R=100k						
3	Analog_IC_Design_Course:LPF_Simulation:1	mag plot				
3	Analog_IC_Design_Course:LPF_Simulation:1	bandwidth	1.588M			
Parameters: R=1M						
4	Analog_IC_Design_Course:LPF_Simulation:1	mag plot				
4	Analog_IC_Design_Course:LPF_Simulation:1	bandwidth	158.8k			

Fig.9 bandwidth values after parametric sweep analysis

3. Pole Zero Analysis:

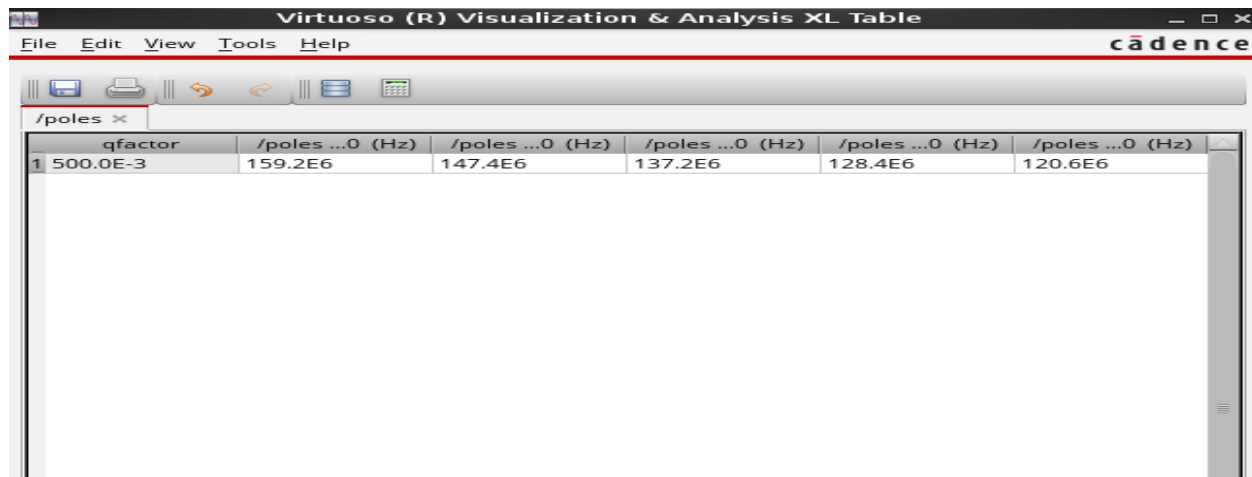

qfactor	/poles ...0 (Hz)	/poles ...0 (Hz)	/poles ...0 (Hz)	/poles ...0 (Hz)	/poles ...0 (Hz)
1 500.0E-3	159.2E6	147.4E6	137.2E6	128.4E6	120.6E6

Fig.10 pole frequency of different values of resistance

Comment: pole frequency analysis is very near to values of different bandwidth in AC analysis above.

Part 2: MOSFET Characteristics

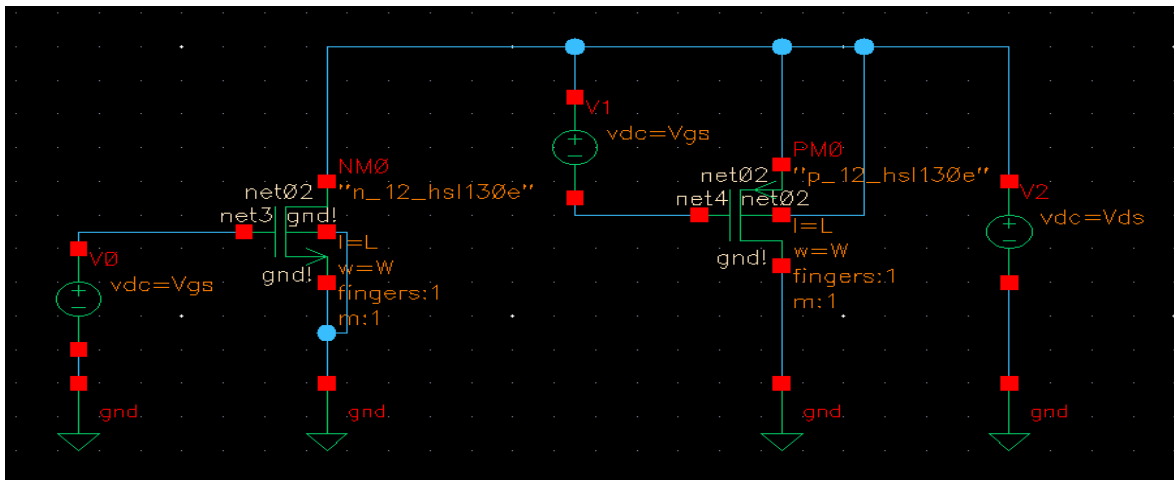


Fig.1 circuit schematic

1. I_D vs V_{GS} :

 


Fig.2 ID vs VGS characteristics for NMOS and PMOS

Comment: as it shown in the previous figure that drain current I_D in long channel MOSFET is higher than the current in short channel MOSFET, and also the current relation in long channel is a quadratic relation but in short channel it's a linear relation and this happen because in short channel drain current is determined by velocity saturation so drain current become proportional to V_{GS} not to V_{GS}^2 as it in long channel MOSFET, and this which affect on current value as that the drain current in short channel is affected by both vertical electric field V_{GS} and lateral electric field V_{DS} which cause velocity saturation in drain current at short channel MOSFET.

Comment: also as it shown in above figure the current in NMOS is higher than that in PMOS this is due to the mobility effect as the mobility of electrons is higher than the mobility of holes so the ratio between drain current in NMOS to that at PMOS equal to ratio between the mobility in electrons to that of holes $\frac{ID_n}{ID_p} = \frac{\mu_n}{\mu_p} = 2 \sim 4$, and also as it appear that the short channel MOSFET act as long channel MOSFET in case of PMOS short channel only affect in case of NMOS.

2. gm vs VGS:

 


Fig.3 gm vs VGS plot from cadence

Comment: as it shown in above figure that gm increases approx. linearly with VGS in long channel as the relation between ID and VGS is a quadratic relation and gm is the change of drain current to change of VGS: $gm = \frac{\partial ID}{\partial VGS}$, and at short channel it can be considered as a step constant change as the relation between ID and VGS is a linear relation due to velocity saturation.

3. ID vs VDS:

 


Fig.4 ID vs VDS for short channel NMOS

 


Fig.5 ID vs VDS for long channel NMOS

Comment: as it shown in above figures that the difference between short channel and long channel NMOS that the steps between different VGS voltage is a quadratic step in long channel and linear steps in short channel due to velocity saturation effect, and we notice that as the value of VGS increase the slope of saturation curve become higher as that the value of VDS_{sat} increase.

4. G_m & r_o vs VDS:

 


Fig.6 r_o vs VDS for short and long channel NMOS

Lab 02

Common Source Amplifier

Part 1: Sizing Chart

For common mode output level we choose: $V_{RD} = \frac{V_{DD}}{2} = 0.6$, so drain resistance will be $R_D = \frac{V_{RD}}{I_D} = \frac{0.6}{100\mu} = 6k\Omega$.

We have a new parameter which is V^* as for real MOSFET case $V_{ov} \neq 2I_D/g_m$, so we have $V^* = \frac{2I_D}{g_m}$, so the desired voltage gain will be $A_v = \frac{2V_{RD}}{V^*} = 5$, so operating amplifier voltage will be $V^* = V_Q^* = \frac{2V_{RD}}{A_v} = 0.24$.

Now we want to determine the width (W) of MOSFET from the following simulation:

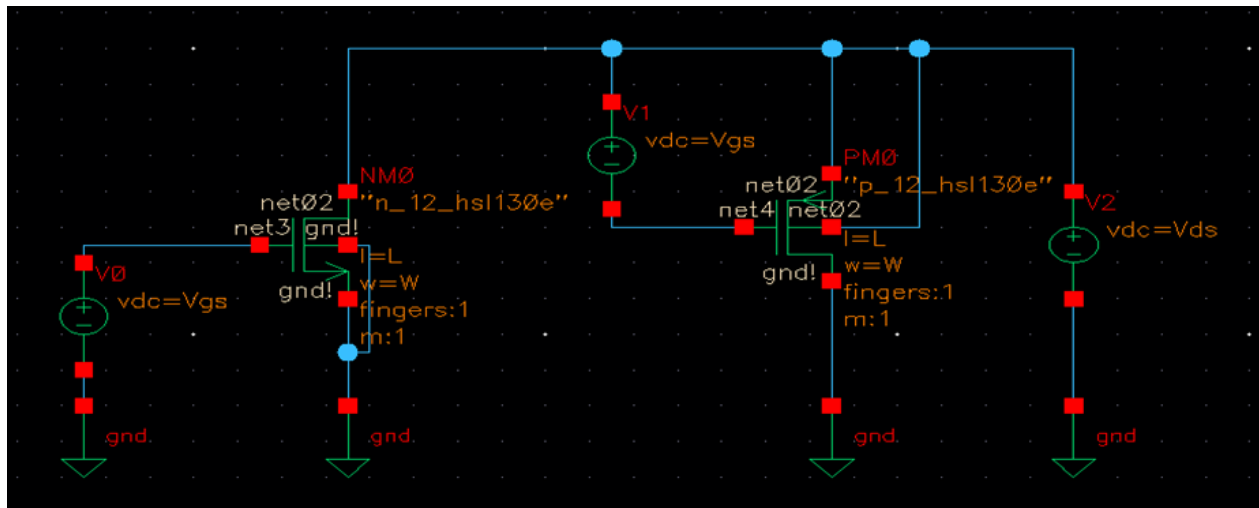


Fig.1 circuit schematic of NMOS and PMOS

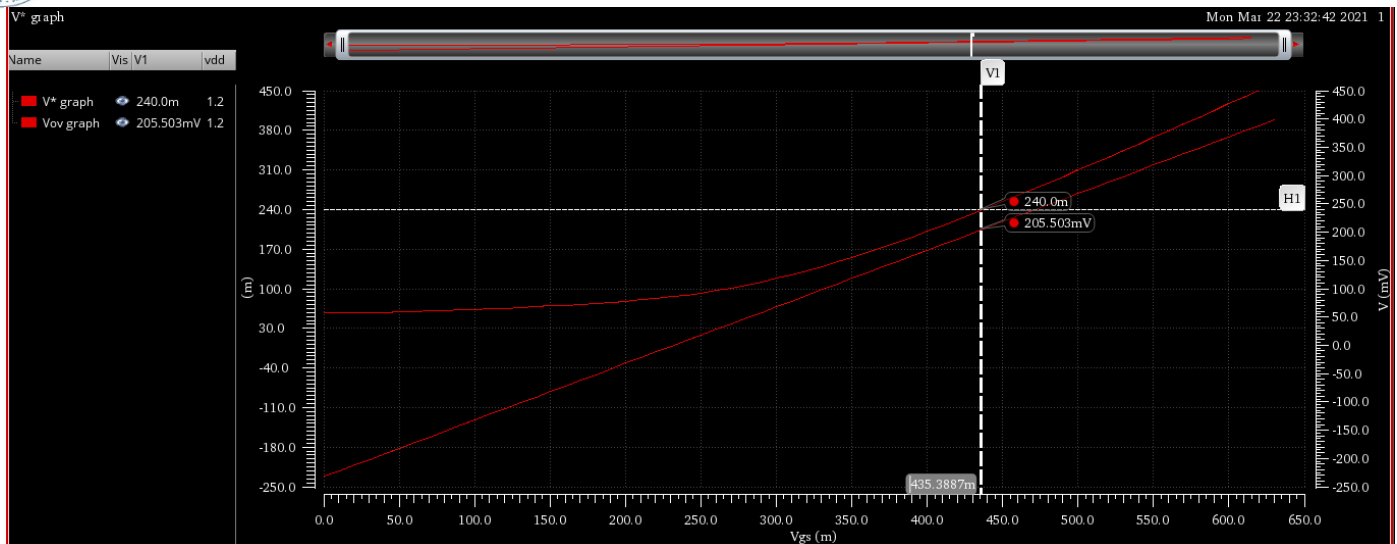


Fig.2 V^* and V_{ov} curves versus V_{gs}

From the previous figure we notice that at the operating voltage of amplifier $V_Q^* = 240mV$, the actual overdrive voltage will be $V_{ovQ} = 205.503mV$, and $V_{GSQ} = 435.3887mV$.

 


Fig.3 I_D , g_m and g_{ds} versus VGS

Now from operating VGS value we get the following operating parameters: $I_{DX} = 52.63uA$, $g_{mX} = 438.395uS$ and $g_{sdX} = 8.55209uS$.

As $I_D \propto W$ and we have at our assumed width in previous simulation: $W = 10uM \rightarrow I_{DX} = 52.63uA$, so using cross multiplication and get width at desired operating current $I_D = 100uA \rightarrow W \cong 20uM$.

Now another check as $g_m \propto W$ at constant overdrive voltage so we get $g_{ds} = 8.974uS$ and $g_m = 875.458uS$ @ $W = 20uM$.

And we have $r_o = \frac{1}{g_{ds}} = 116.96k\Omega$. so now we could calculate voltage gain $A_v = g_m *$

$$\left(\frac{R_D * r_o}{R_D + r_o} \right) = 4.9.$$

Part 2: CS Amplifier

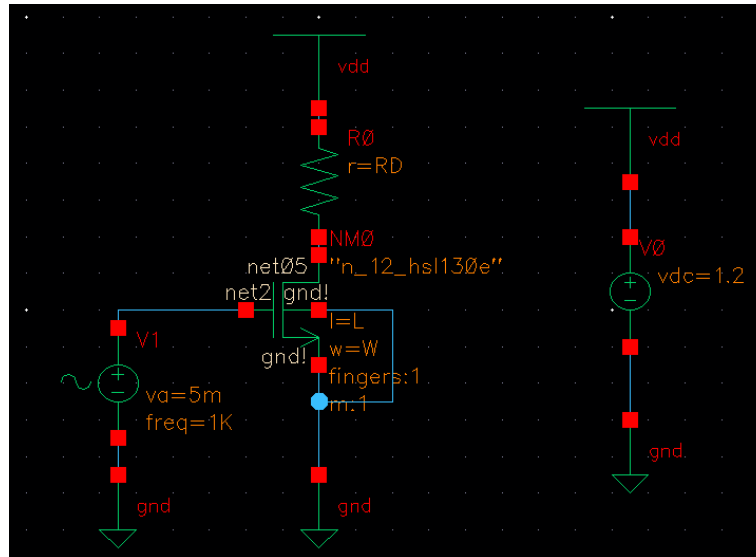


Fig.1 CS Amplifier circuit schematic

1. OP and AC analysis:

 


Fig.2 input signal and output signal after amplification

Test	Output	Nominal	Spec	Weight	Pass/Fail
Analog_IC_Design_Course:CS_Amp:1	output				
Analog_IC_Design_Course:CS_Amp:1	input				
Analog_IC_Design_Course:CS_Amp:1	NM0:gm	883.6u			
Analog_IC_Design_Course:CS_Amp:1	NM0:gds	9.319u			
Analog_IC_Design_Course:CS_Amp:1	NM0:id	106.7u			
Analog_IC_Design_Course:CS_Amp:1	NM0:vth	228.4m			
Analog_IC_Design_Course:CS_Amp:1	ro	107.3k			
Analog_IC_Design_Course:CS_Amp:1	gm*ro	94.81			
Analog_IC_Design_Course:CS_Amp:1	amp-gain	5.301			

Fig.3 results from simulation for operating parameters

As shown in above figure that the results from CS simulation is nearly to our actual values from simulation in part 1.

- We see that r_o is much larger than R_D so assumption of ignoring r_o is justified in this case as this is a parallel connection of resistors, but in case of short channel r_o become more controlled by VDS so the value of r_o decrease and the assumption not justified in this case.
- Intrinsic gain will be: $g_m * r_o = 94.81$.
- Amplifier gain will be: $A_v = 5.3$.
- As it shown that the intrinsic gain of single transistor is much larger than the amplifier gain.

 


Fig.4 amplifier gain versus frequency from AC analysis

2. Gain Non-Linearity:

 


Fig.5 static characterization of the amplifier VOUT vs VIN

Comment: as shown in the previous figure that the static gain isn't linear and this because of g_m as that the gain equation is: $A_v \cong g_m * R_D$ and g_m is a strong function of input voltage VGS which cause non-linearity.

 


Fig.6 derivative of output voltage versus input voltage VGS

 


Fig.7 g_m versus time after transient analysis

Comment: from above simulations it's clear that the gain is not linear as it is function in g_m which is function in its turn in input voltage VIN "VGS" and it shown in the transient analysis of g_m as it changes with time as shown in above figure.

3. Maximum Gain:

 


Fig.8 voltage gain A_v versus R_D AC analysis

Comment: as shown in above figure that the gain increase with change of R_D but then decrease and this happen because of the increase of value of R_D as the actual relation of voltage gain: $A_v = g_m * (R_D \parallel r_o)$ so by increasing the value of R_D it becomes more comparable with r_o so this parallel connection decreases the value of total resistance which decrease the gain as shown in above figure.

So as shown that the highest gain will be: $A_v = 6.2$ and the value of drain resistance which give this gain will be: $R_D = 8K$.

Max gain calculated in part 1: $A_v = 4.9 = g_m * R_D$ and the value of $g_m = 883.5\mu S$, so $R_D = 5.5kohms$.

The available swing of output maximum gain will equal: $V_{dd} - V_{RD} - V_{ov} = 1.2 - 106\mu * 8k - 435.38m + 228.4m = 0.145 volts$.

From previous conclusions the scaling down of supply voltage VDD affects on output swing which also affect on gain.

Lab 03

Cascode Amplifier

Part 1: Sizing Chart

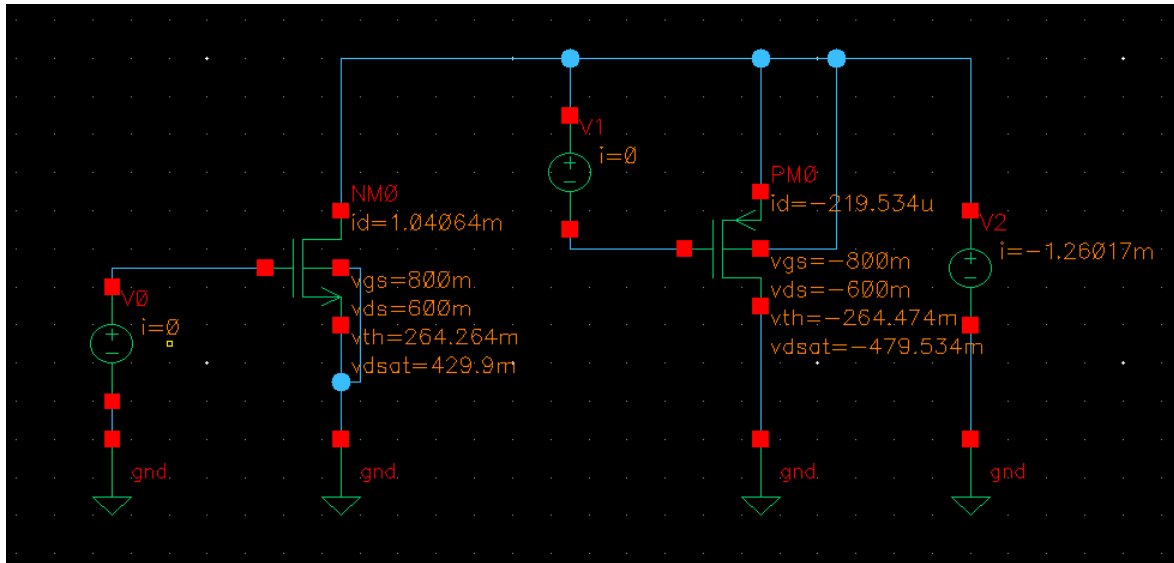


Fig.1 testbench circuit for NMOS OP parameters

 


Fig.2 V^* and V_{ov} versus V_{GS}

Comment: we find from the previous figure's simulation the following results at $V_Q^* = 200mV \rightarrow V_{ovQ} = 157.8526mV, V_{GSQ} = 422.1171mV$.

 


Fig.3 gm, id and gds versus VGS

Comment: we get values at $V_{gsQ} = 422.1171mV \rightarrow g_m = 1.408m, g_{ds} = 30.7468u$ and $I_D = 148.115uA$.

As current is proportional to width use cross multiplication to get actual width at $I_D = 20uA \rightarrow W = 1.35um$.

Part 2: CASCODE for Gain

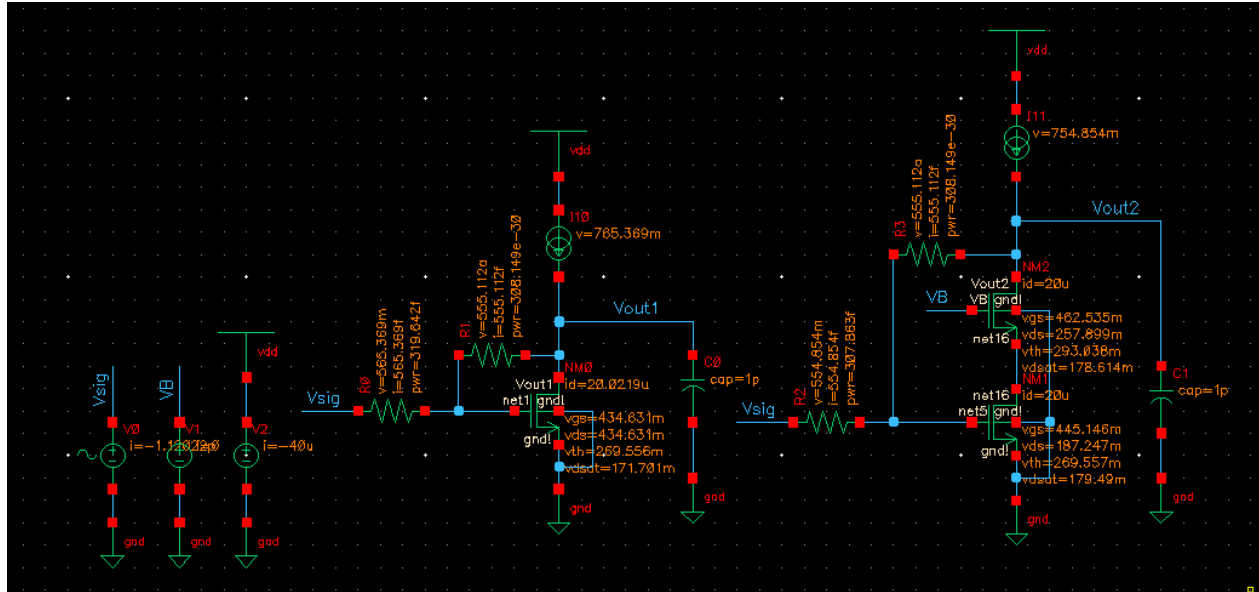


Fig.1 Circuit schematic for cascode and CS amplifiers with OP parameters

1.OP Analysis:

Now we want to choose the value of cascode bias voltage VB at $V_{DS} = V_{ovQ} + 100m = 257.8526m$ so from the following figure we choose $V_B = 649.782mV$.

 


Fig.2 DC sweep for cascode bias voltage versus VDS to get suitable VB



Test	Output	Nominal	Spec
Analog_IC_Design_Course:Cascode_Amp:1	NM0:id	20.02u	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:vgs	434.6m	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:vds	434.6m	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:vth	269.6m	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:vdsat	171.7m	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:gm	194u	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:gds	4.519u	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:gmb	25.15u	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:cdb	-689.3a	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:cgd	-398.1a	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:cgs	-5.166f	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:csb	-1.449f	
Analog_IC_Design_Course:Cascode_Amp:1	NM0:region	2	

Fig.3 OP parameters of MOSFET at CS amplifier NM0

Test	Output	Nominal	Spec
Analog_IC_Design_Course:Cascode_Amp:1	NM1:id	20u	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:vgs	445.1m	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:vds	187.2m	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:vth	269.6m	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:vdsat	179.5m	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:gm	173.7u	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:gds	24.03u	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:gmb	22.86u	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:cdb	-811.2a	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:cgd	-528.8a	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:cgs	-5.19f	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:csb	-1.442f	
Analog_IC_Design_Course:Cascode_Amp:1	NM1:region	2	

Fig.4 OP parameters of cascode MOSFET NM1

Test	Output	Nominal	Spec
Analog_IC_Design_Course:Cascode_Amp:1	NM2:id	20u	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:vgs	462.5m	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:vds	257.9m	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:vth	293m	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:vdsat	178.6m	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:gm	187.1u	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:gds	8.633u	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:gmb	21.39u	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:cdb	-695.3a	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:cgd	-435.2a	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:cgs	-5.164f	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:csb	-1.266f	
Analog_IC_Design_Course:Cascode_Amp:1	NM2:region	2	

Fig.5 OP parameters of cascode MOSFET NM2

Comment.1: VTH of MOSFET NM0 and NM1 are the same and not suffer from body effect as the source and bulk are directly connected to GND, but the value of VTH of NM2 is different as it's suffer from body effect as the source isn't connected to GND so there is value for VBS which increase threshold voltage of NM2.

Comment.2: as it shown that all MOSFETs are in saturation region which is equivalent to value 2 at region simulation in cadence.

Comment.3: a) $G_m > G_{ds}$ b) $G_m > G_{mb}$ c) $|C_{gs}| \gg |C_{gd}|$ d) $|C_{sb}| \gg |C_{db}|$

2.AC Analysis:



Test	Output	Nominal	Spec
Analog_IC_Design_Course:Cascode_Amp:1	dB20(VF("/Vout1"))		
Analog_IC_Design_Course:Cascode_Amp:1	ymin(dB20(VF("/Vout1")))	32.65	
Analog_IC_Design_Course:Cascode_Amp:1	ymax(mag(VF("/Vout1")))	42.93	
Analog_IC_Design_Course:Cascode_Amp:1	bandwidth(VF("/Vout1") 3 "lo...	718.9k	
Analog_IC_Design_Course:Cascode_Amp:1	gainBwProd(VF("/Vout1"))	30.93M	
Analog_IC_Design_Course:Cascode_Amp:1	dB20(VF("/Vout2"))		
Analog_IC_Design_Course:Cascode_Amp:1	ymin(dB20(VF("/Vout2")))	45.19	
Analog_IC_Design_Course:Cascode_Amp:1	ymax(mag(VF("/Vout2")))	181.8	
Analog_IC_Design_Course:Cascode_Amp:1	bandwidth(VF("/Vout2") 3 "lo...	136.8k	
Analog_IC_Design_Course:Cascode_Amp:1	gainBwProd(VF("/Vout2"))	24.94M	

Fig.6 simulation results of AC analysis for CS amplifier and CASCODE amplifier

 


Fig.7 CS and CASCODE amplifiers gain in DB

 


Fig.8 CS and CASCODE gain magnitude

Part 3: CASCODE for BW

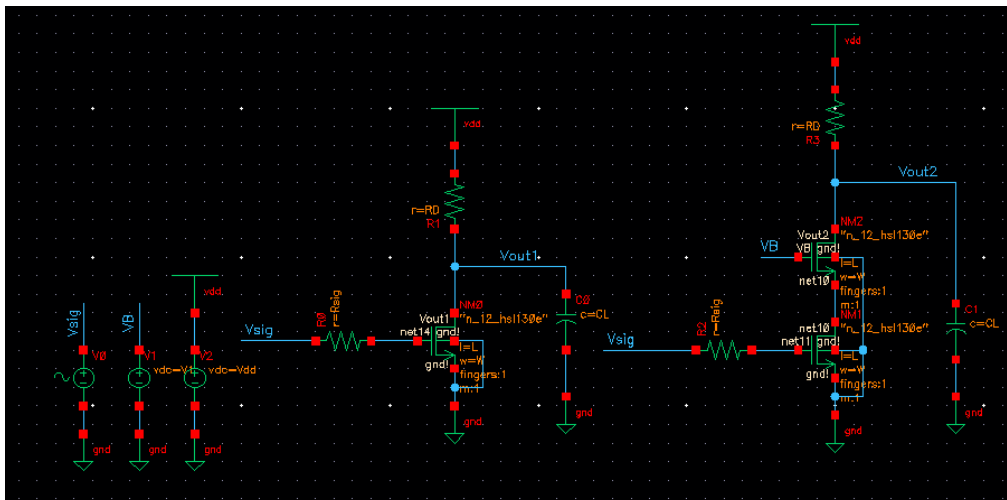




Fig.1 Circuit schematic for CASCODE and CS amplifier after replacing current source by RD

1.OP Analysis:

Hint: as we want voltage drop on RD as following $V_{RD} = V_{dd}/2 = 0.6$ and the value of current is $I_d \cong 20\mu A$ so we will set the value of resistance $R_D = \frac{V_{RD}}{I_D} = 30Kohms$.

Test	Output	Nominal	Spec	Weight	Pass/Fail
Analog_Course:Cascode_BW:1	NM0:id	18.48u			
Analog_Course:Cascode_BW:1	NM0:vgs	422.1m			
Analog_Course:Cascode_BW:1	NM0:vds	645.6m			
Analog_Course:Cascode_BW:1	NM0:vth	269.6m			
Analog_Course:Cascode_BW:1	NM0:vdsat	162.5m			
Analog_Course:Cascode_BW:1	NM0:gm	189.7u			
Analog_Course:Cascode_BW:1	NM0:gds	3.751u			
Analog_Course:Cascode_BW:1	NM0:gmb	24.48u			
Analog_Course:Cascode_BW:1	NM0:cdb	-635.8a			
Analog_Course:Cascode_BW:1	NM0:cgd	-393.1a			
Analog_Course:Cascode_BW:1	NM0:cgs	-5.117f			
Analog_Course:Cascode_BW:1	NM0:csb	-1.446f			
Analog_Course:Cascode_BW:1	NM0:region	2			

Fig.2 OP parameters of MOSFET of CS amplifier

Test	Output	Nominal	Spec	Weight	Pass/Fail
Analog_Course:Cascode_BW:1	NM1:id	18.29u			
Analog_Course:Cascode_BW:1	NM1:vgs	422.1m			
Analog_Course:Cascode_BW:1	NM1:vds	209.4m			
Analog_Course:Cascode_BW:1	NM1:vth	269.6m			
Analog_Course:Cascode_BW:1	NM1:vdsat	162.3m			
Analog_Course:Cascode_BW:1	NM1:gm	185.9u			
Analog_Course:Cascode_BW:1	NM1:gds	12.09u			
Analog_Course:Cascode_BW:1	NM1:gmb	24.31u			
Analog_Course:Cascode_BW:1	NM1:cdb	-868a			
Analog_Course:Cascode_BW:1	NM1:cgd	-512a			
Analog_Course:Cascode_BW:1	NM1:cgs	-5.692f			
Analog_Course:Cascode_BW:1	NM1:csb	-1.594f			
Analog_Course:Cascode_BW:1	NM1:region	2			

Fig.3 OP parameters of 1st MOSFET of CASCODE amplifier



Test	Output	Nominal	Spec	Weight	Pass/Fail
Analog_Course:Cascode_BW:1	NM2:ids	18.3u			
Analog_Course:Cascode_BW:1	NM2:vgss	440.4m			
Analog_Course:Cascode_BW:1	NM2:vds	442m			
Analog_Course:Cascode_BW:1	NM2:vth	295.8m			
Analog_Course:Cascode_BW:1	NM2:vdsat	160.2m			
Analog_Course:Cascode_BW:1	NM2:gms	196.5u			
Analog_Course:Cascode_BW:1	NM2:gds	4.303u			
Analog_Course:Cascode_BW:1	NM2:gmb	22.08u			
Analog_Course:Cascode_BW:1	NM2:cdb	-699.9a			
Analog_Course:Cascode_BW:1	NM2:cgd	-440.9a			
Analog_Course:Cascode_BW:1	NM2:cgs	-5.632f			
Analog_Course:Cascode_BW:1	NM2:csb	-1.378f			
Analog_Course:Cascode_BW:1	NM2:region	2			

Fig.4 OP parameters of 2nd CASCODE amplifier

Comment: as shown from above simulation results the MOSFETs of CS and CASCODE amplifier are been set at saturation region (region=2).

2.AC Analysis:

Test	Output	Nominal	Spec	Weight	Pass/Fail
Analog_Course:Cascode_BW:1	CS DC gain	5.573			
Analog_Course:Cascode_BW:1	CS BW	1.78M			
Analog_Course:Cascode_BW:1	CS GBW	9.944M			
Analog_Course:Cascode_BW:1	CS UGF	9.794M			
Analog_Course:Cascode_BW:1	Cascode DC gain	5.253			
Analog_Course:Cascode_BW:1	Cascode BW	2.264M			
Analog_Course:Cascode_BW:1	Cascode GBW	11.92M			
Analog_Course:Cascode_BW:1	Cascode UGF	11.79M			

Fig.5 AC simulation results of CS and CASCODE amplifiers

Comment: as shown from above results that the gain of CASCODE is the same gain of CS amplifier and this is due to the effect of RD value, but CASCODE in this case is very useful for bandwidth as shown in above figure.

 


Fig.6 magnitude bode plot for CS and CASCODE amplifiers

Lab 04

Common Drain Frequency Response

Part 1: Sizing Chart

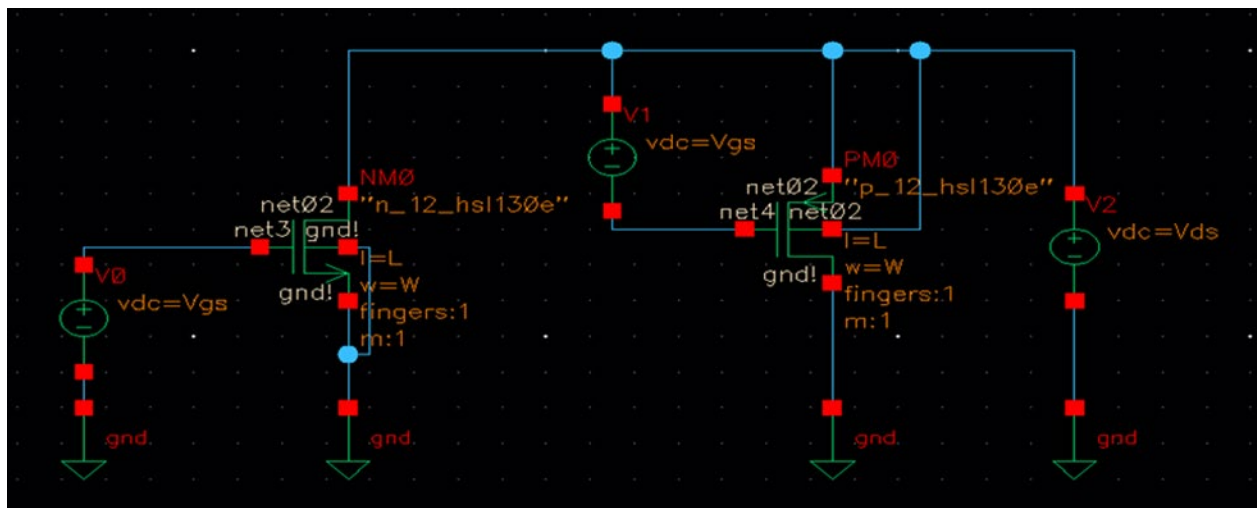


Fig.1 PMOS and NMOS circuit schematic for sizing

From simulations results we see that the value of PMOS threshold voltage: $V_{th} = -256.638\text{mv}$, so now set the value of VGS at $V_{GS} = -0.656638\text{v}$, and as we have $|V_Q^*| = 200\text{mv}$, so now from the following graph set $|V_{GSQ}| = 428.3391\text{mv}$ and $|V_{ovQ}| = 171.7014\text{mv}$.

 


Fig.2 VGS and VOV results from simulation at $V^*=200\text{mV}$

 


Fig.3 the actual values of I_D , g_m and g_{ds} at V_{GSQ}

It's known that at constant $V_{ov} \rightarrow I_D \propto W$ and we have assumed $W=10\mu\text{m}$ which gives $I_D = 14.434\mu\text{A}$, so by using cross multiplication at $I_D = 10\mu\text{A} \rightarrow W = 6.93\mu\text{m}$.

And we have $g_m, g_{ds} \propto 1/W$, so using cross multiplication we get the values of g_m and g_{ds} at $W=6.93\mu\text{m}$ which are $g_m = 100\mu$ and $g_{ds} = 441.2\text{n}$.

Part 2: CD Amplifier

1.OP (Operating Point) Analysis:

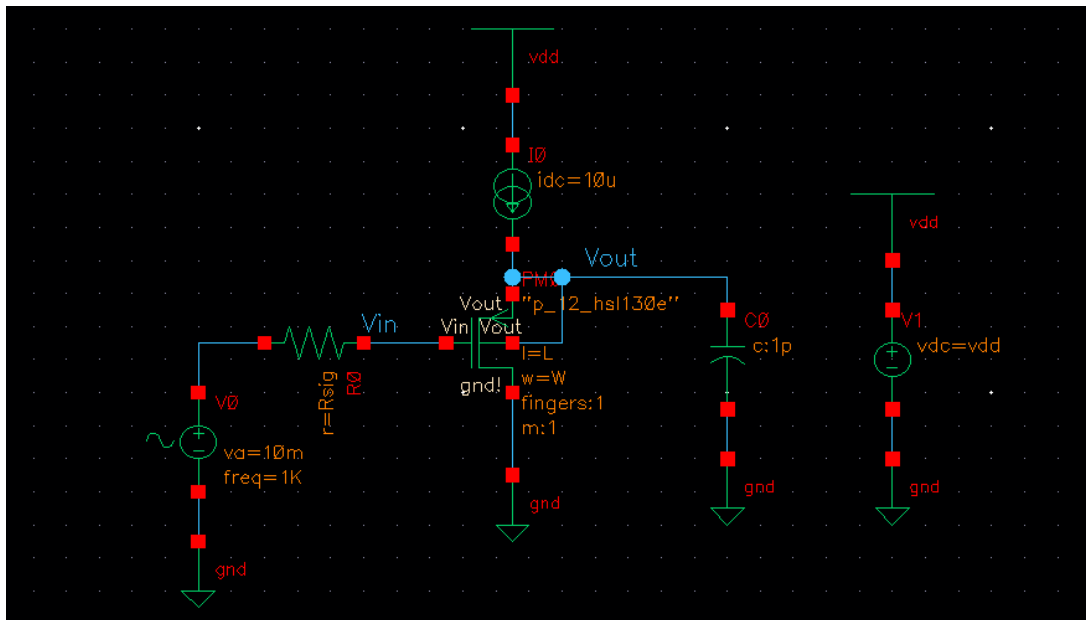


Fig.1 Common Drain Circuit schematic

Test	Output	Nominal	Spec
Analog_IC_Design_Course:CD_Freq:1	id	-10u	
Analog_IC_Design_Course:CD_Freq:1	vgs	-427.5m	
Analog_IC_Design_Course:CD_Freq:1	vds	-855.8m	
Analog_IC_Design_Course:CD_Freq:1	vth	-256.6m	
Analog_IC_Design_Course:CD_Freq:1	vdsat	-164.4m	
Analog_IC_Design_Course:CD_Freq:1	gm	100.3u	
Analog_IC_Design_Course:CD_Freq:1	gds	422.1n	
Analog_IC_Design_Course:CD_Freq:1	gmb	20.95u	
Analog_IC_Design_Course:CD_Freq:1	cdb	-4.42f	
Analog_IC_Design_Course:CD_Freq:1	cgd	-2.154f	
Analog_IC_Design_Course:CD_Freq:1	cgs	-52.57f	
Analog_IC_Design_Course:CD_Freq:1	csb	-15.01f	
Analog_IC_Design_Course:CD_Freq:1	region	2	

Fig.2 OP parameters of CD amplifier

Comment: as shown in above figure that common drain in region 2 which mean that it's in saturation case.

2.AC Analysis:

 


Fig.3 bode plot magnitude of VOUT at CD amplifier

Comment: as shown on above figure that there is a peaking in frequency domain in case of CD amplifier, so the value of maximum gain in this case will be: $A_v = 5.798$.

Analytical solution for quality factor Q for CD amplifier: as we know that we can't use miller approximations and OCTC techniques because it doesn't give dominant and non-dominant poles but only give us all poles at high frequency so we use exact solution in this case with some special cases that as we use IDC so R_s will be very high and can be neglected and as we use PMOS so there is no body effect and can neglect CLM also.

Now we have $b_1 = \left(\frac{(c_{gs} + c_{gd})c_L + c_{gs}c_{gd}}{g_m} \right) R_{sig} = 2.18f$, $b_2 = c_{gd}R_{sig} + \frac{c_{gs} + c_L}{g_m} =$

$24.77n$ and $Q = \frac{\sqrt{b_1}}{b_2} = 1.88$, so from previous analysis we have $Q > 0.5$ which mean

underdamped case which cause peaking in frequency domain and ringing in time domain.

 


Fig.2 bode plot magnitude after sweep of CL

 


Fig.3 peaking versus CL sweep

Comment: as shown from previous simulation results that as the load capacitance increases the peaking value decreases as the quality factor is inverse proportional to load capacitance.

 


Fig.4 bode plot magnitude after sweep of RSIG

 


Fig.5 peaking versus RSIG sweep

Comment: from previous figure as it shown that as we increase RSIG the value of peaking increase as the quality factor Q is directly proportional with RSIG.

3. Transient Analysis:

 


Fig.6 VIN & VOUT versus time at transient analysis

DC shift between input signal and output signal is equal to VGS which is equal:

$DC\ shift = VGS = 428.3391mV$, and the output signal is shifted up as we use PMOS if we want to shift output signal down we can use NMOS CD amplifier.

It's clear the effect of ringing on input and output signals and using cadence calculator, we evaluate the value of overshoot in percentage which will be **41.2%**.

 


Fig.7 VOUT transient analysis versus sweep pf CL

 


Fig.8 overshoot versus CL

 


Fig.9 VOUT transient analysis versus sweep of RSIG

 


Fig.10 overshoot versus sweep of R_{SIG}

Lab 05

Simple VS Low Compliance Cascode Current Mirror

Part 1: Sizing Chart

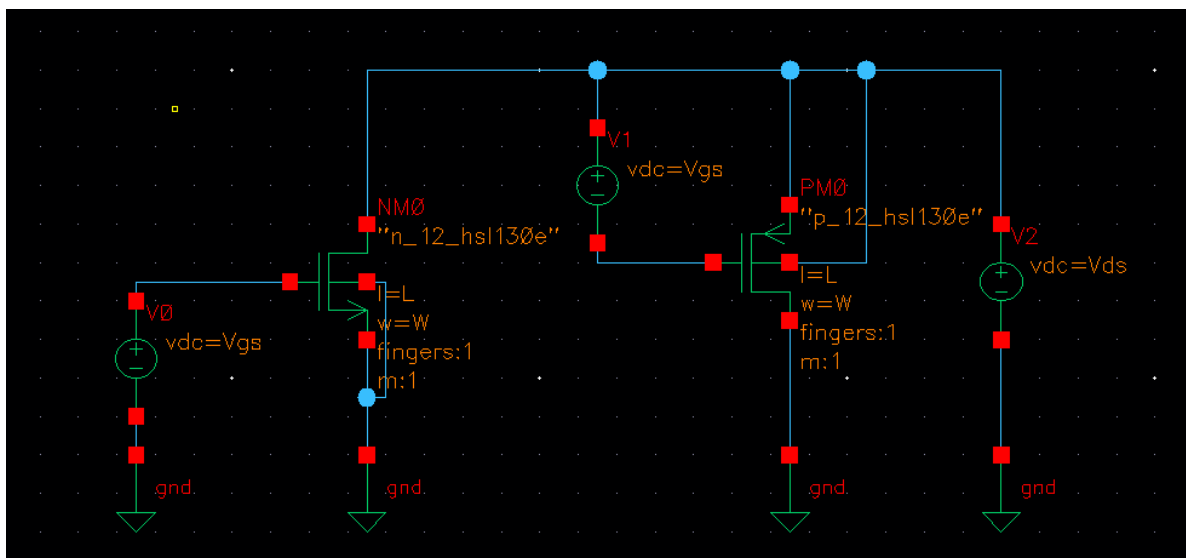


Fig.1 PMOS and NMOS circuit schematic for sizing

We have set the real MOSFET overdrive voltage as following: $V^* = 200mV$.

 


Fig.2 VGS and VOV results from simulation at $V^*=200mV$

So as the previous figure we get the following: $V_{gsQ} = 404.5539mV$, $V_{ovQ} = 163.0285mV$.

 


Fig.3 the actual values of ID, gm and gds at VGSQ

So we get now the actual value of drain current at assumed width ($W=10\mu m$) which will be $ID=73.9639\mu A$ and as the current is always proportional to width of MOSFET so we can get the actual width at $ID=20\mu A$ which will be $W=2.7\mu m$.

Part 2: Current Mirror

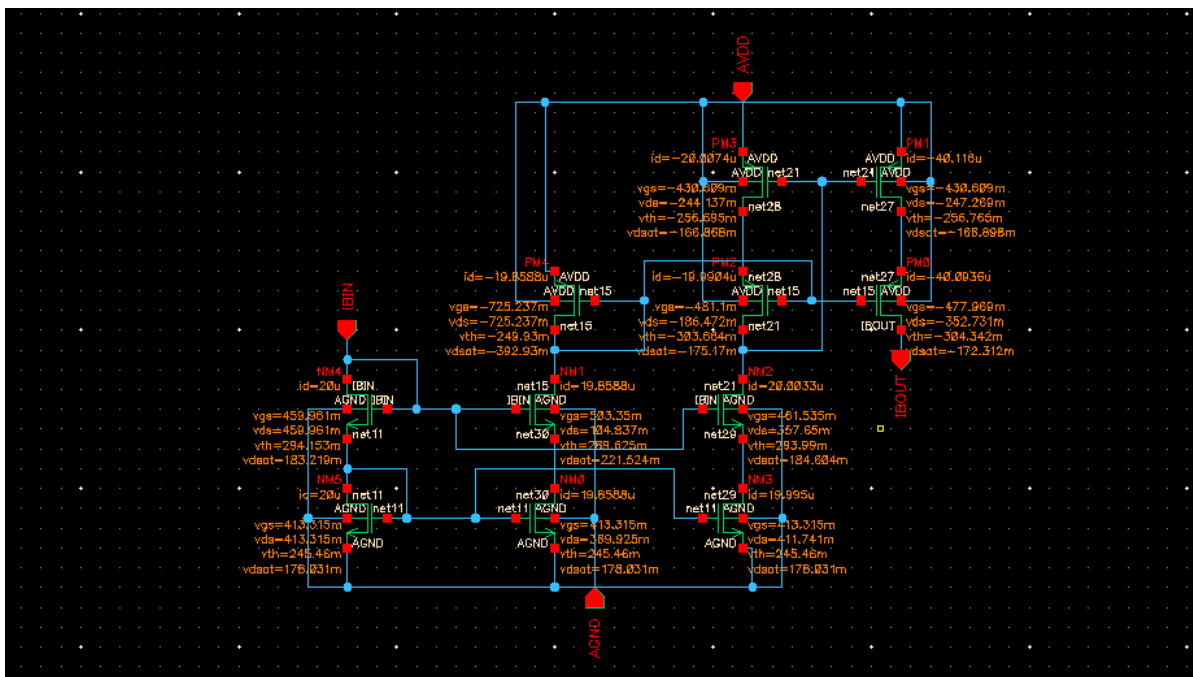


Fig.1 wide sense current mirror circuit schematic

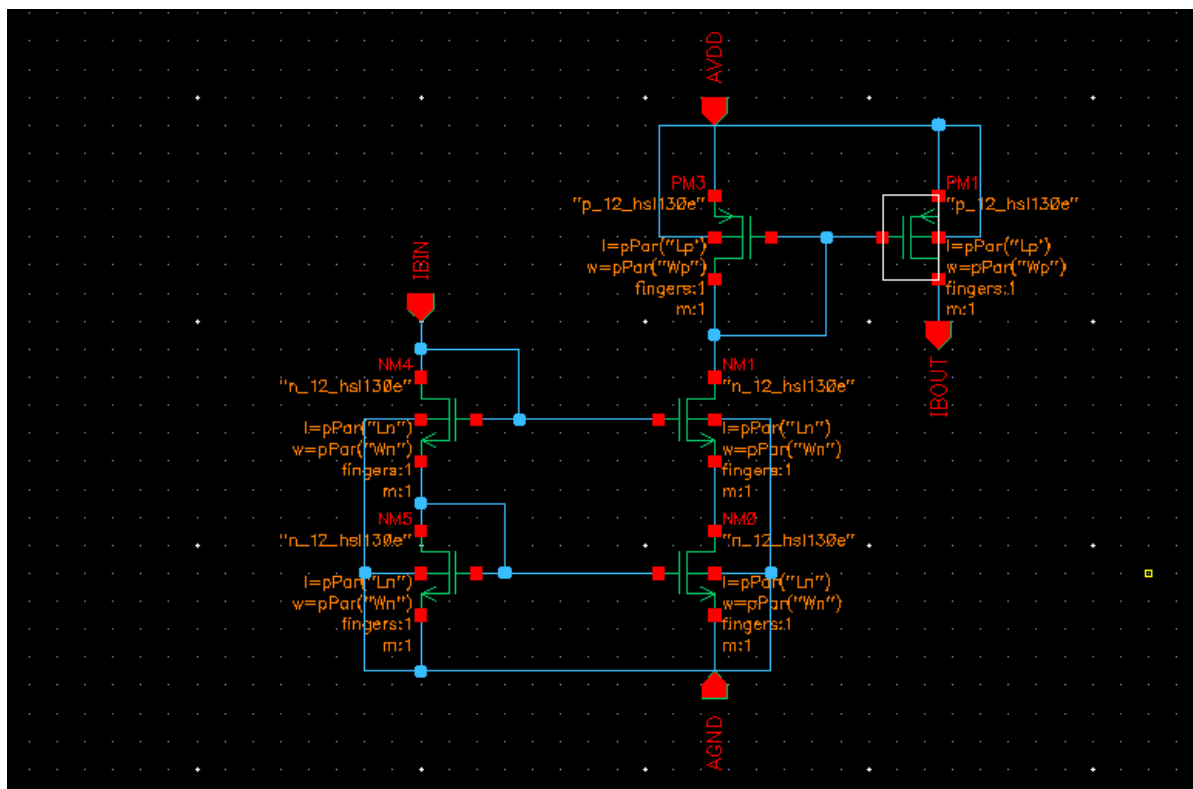


Fig.2 simple current mirror circuit schematic

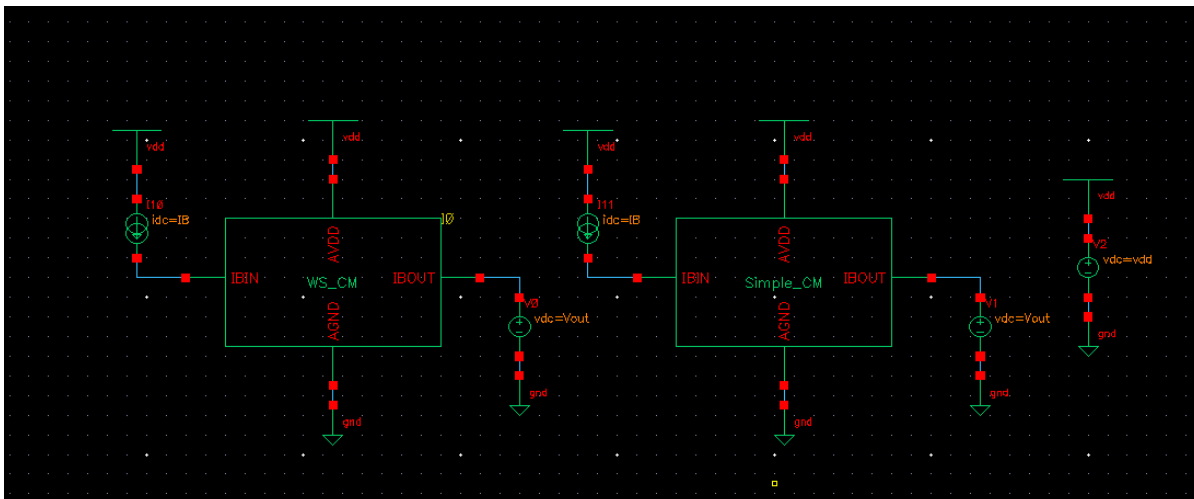


Fig.3 testbench for CMs circuit schematic

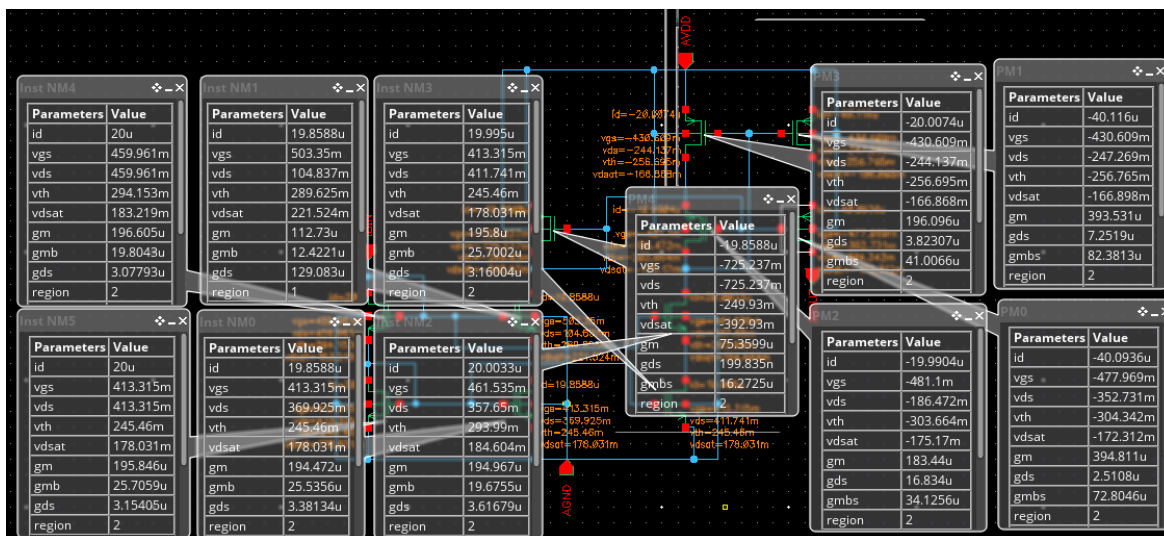


Fig.4 operating point parameters of WS CM MOSFETs

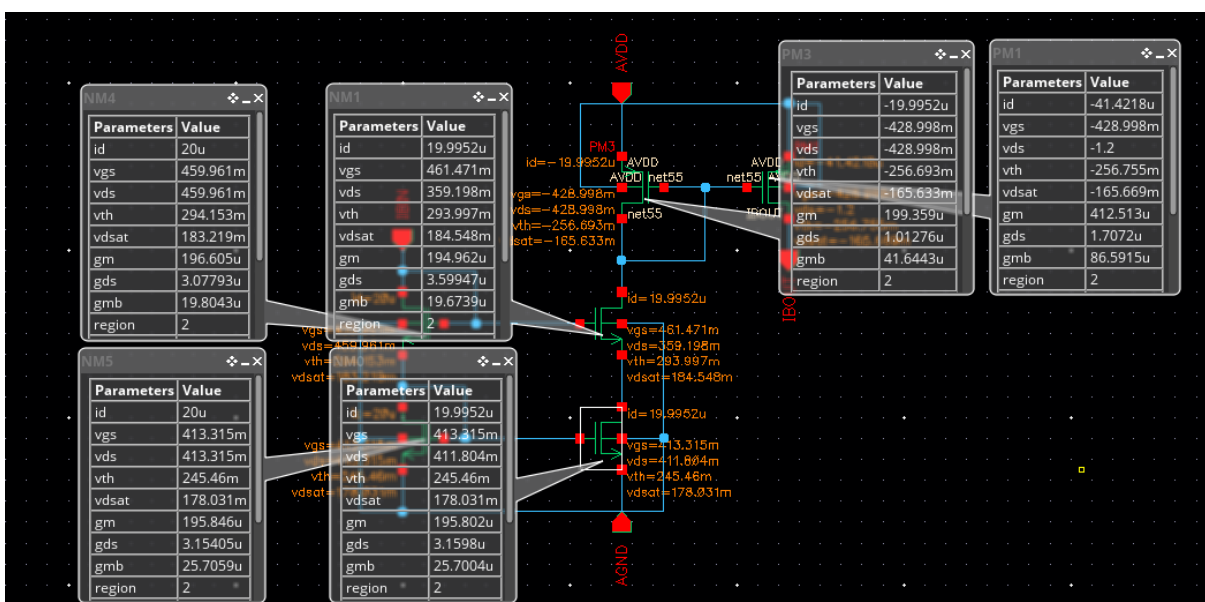


Fig.5 operating point parameters of simple CM MOSFETs

 


Fig.6 IB out versus VOUT from two CMs

Comment: the difference between two CMs that simple cascode CM wastes the headroom of supply voltage due to extra V_{TH} in the 2nd MOSFET but at wide sense CM there is no wasting of supply voltage as diode connected over two MOSFETs.

 


Fig.7 IB out versus VOUT at 1 volt for two CMs

Comment: from the shown figure error percentage of WS CM will be 7.4%, and error percentage of simple CM will be 3.33%.

So simple cascode CM is more accurate but it wastes a lot from supply voltage.

Test	Output	Nominal	Spec
Analog_IC_Design_Course:lab_05_cm_tb:1	WS		
Analog_IC_Design_Course:lab_05_cm_tb:1	Simple		
Analog_IC_Design_Course:lab_05_cm_tb:1	Simple CM	97.33	
Analog_IC_Design_Course:lab_05_cm_tb:1	WS CM	92.68	

Fig.8 error results of two CMs from ADL simulation

 


Fig.9 Rout versus VOUT of two CMs

 


Fig.10 Rout versus VOUT of two CMs log scale