

# Lab 02

## Common Source Amplifier

### Part 1: Sizing Chart

- For real MOSFET  $V_{ov} \neq \frac{2I_D}{g_m}$ , so we define expression  $V^* = \frac{2I_D}{g_m}$ , and  $V_{ov} = V^*$  in case of square law MOSFET only.

So actual gain will be  $A_v = \frac{2V_{RD}}{V^*} = \frac{2I_D R_D}{V^*}$ .

- And we assume that channel length value will be  $L=2\mu m$ , to avoid short channel effects.
- We choose the value of  $V_{RD} = V_{DD}/2 = 0.9V$ , which is a common mode output level voltage.
- We have  $I_D = 50\mu A \rightarrow \therefore R_D = \frac{V_{RD}}{I_D} = 18k\Omega$ .
- Also we have  $A_v = -10 \rightarrow \therefore V^* = \frac{2V_{RD}}{A_v} = 0.18V$ , which we make the OP voltage of real MOSFET overdrive voltage:  $V_Q^* = 0.18V$ .
- Calculations of MOSFET width (W) from cadence:

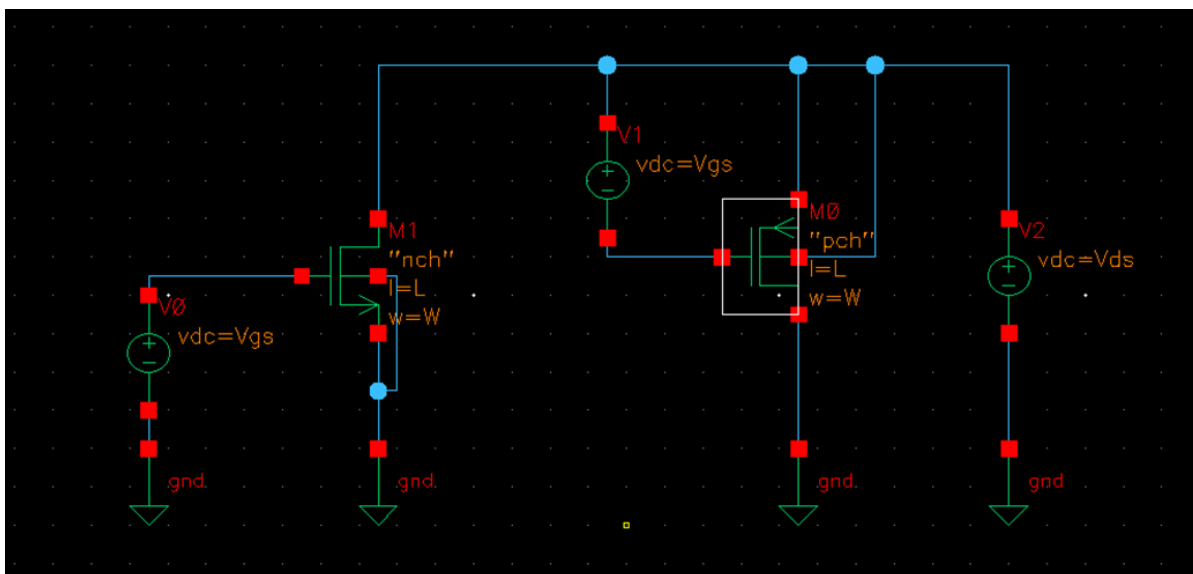


Fig.1 Circuit -schematic from cadence used for selecting MOSFET width

After DC simulation we found that value of threshold voltage will be  $V_{th} = 382.625mV$ .

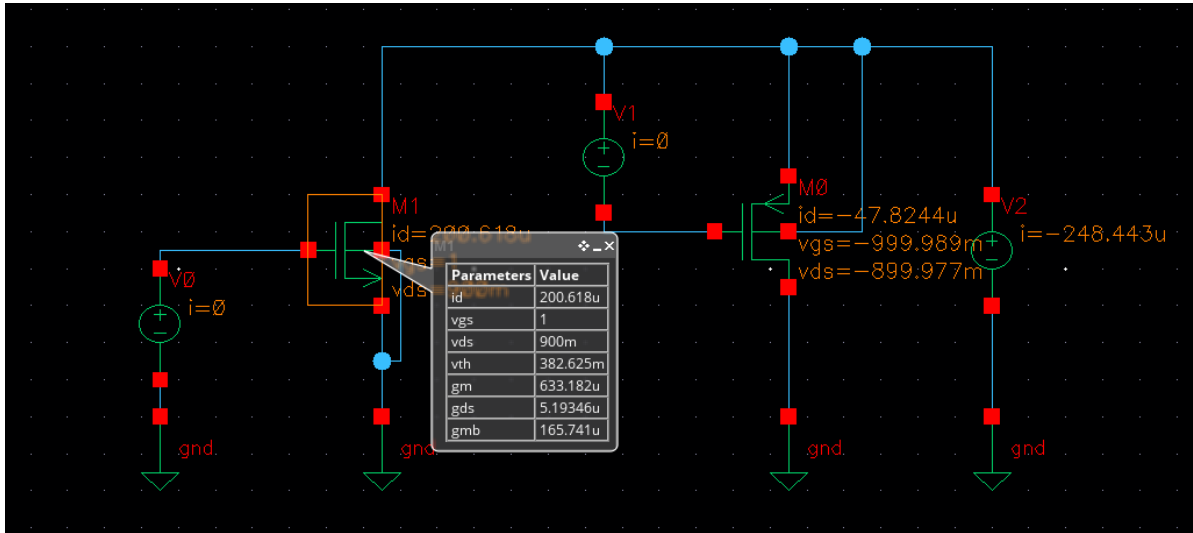


Fig.2 Circuit schematic from cadence

So select to sweep  $V_{gs} = 0 \rightarrow V_{th} + 0.4 = 0 \rightarrow 782.625mV$ , and select  $V_{ds} = \frac{V_{DD}}{2} = 0.9V$ .

And firstly assume the width of MOSFET to be  $W=10\mu m$ ,  $L=2\mu m$ .

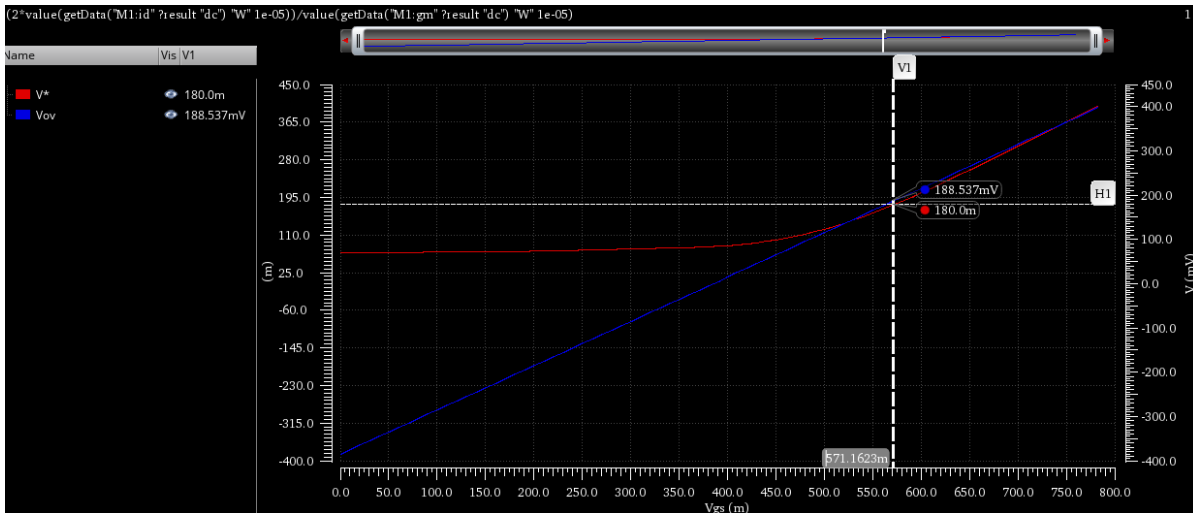


Fig.3  $V_{ov}$  &  $V^*$  versus  $V_{gs}$

So we found values of  $V_{gsQ} = 571.1623mV$ ,  $V_{ovQ} = 188.537mV$ , at value  $V_Q^* = 180mV$ .

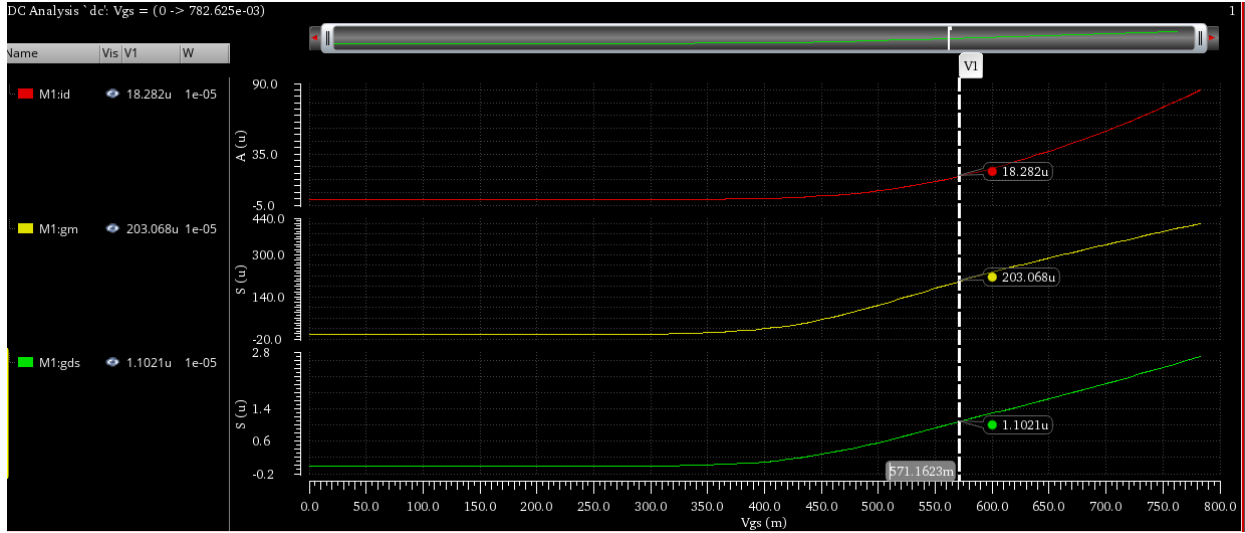


Fig.4  $I_D$ ,  $g_m$  and  $g_{ds}$  versus  $V_{gs}$

As shown in previous simulation results that at operating point

$V_{gs} = 571.1623\text{mV}$ , we have the following results

$I_{dQ} = 18.282\mu\text{A}$ ,  $g_{mQ} = 203.068\mu\text{S}$  and  $g_{dsQ} = 1.1021\mu\text{S}$ .

Parameter	Value
$V_Q^*$	180mV
$V_{gsQ}$	571.1623mV
$V_{ovQ}$	188.537mV
$I_{dQ}$	18.282uA
$g_{mQ}$	203.068uS
$g_{dsQ}$	1.1021uS

Now return to our assumption of width of MOSFET  $W=10\mu\text{m}$ , and as we know that  $I_D \propto W$  at any instant even square law is valid or not.

So at  $W = 10\mu\text{m} \rightarrow I_{DQ} = 18.282\mu\text{A}$ , using the cross multiplication we can get width value at  $I_{DQ} = 50\mu\text{A}$  which will be  $W=27.35\mu\text{m}$ .

And also width of MOSFET is proportional to  $g_m$  and  $g_{ds}$ , at  $W = 10\mu\text{m} \rightarrow g_{mQ} = 203.068\mu\text{S}$  and  $g_{dsQ} = 1.1021\mu\text{S}$ , so using cross multiplication we can get values of  $g_{mQ}$  and  $g_{dsQ}$ , which will be as following:

$W = 27.35\mu\text{m} \rightarrow g_{mQ} = 555.39\mu\text{S}$  and  $g_{dsQ} = 3.014\mu\text{S}$ .

And since  $r_o = \frac{1}{g_{dsQ}} = 331.785\text{k}\Omega$ .

So Common Source Parameters:

Parameter	Value
L	2um
W	27.35um
$V_{gsQ}$	571.1623mV
$R_D$	18k $\Omega$
$I_{DQ}$	50uA
$g_m$	555.39uS
$g_{ds}$	3.014uS
$r_o$	331.785k $\Omega$

Check:  $A_v = g_m * (R_D \parallel r_o) = 9.48$ .

## Part 2: CS Amplifier

### 1.OP and AC Analysis:

- Operating point parameters comparison from CS simulation and our results in part 1:

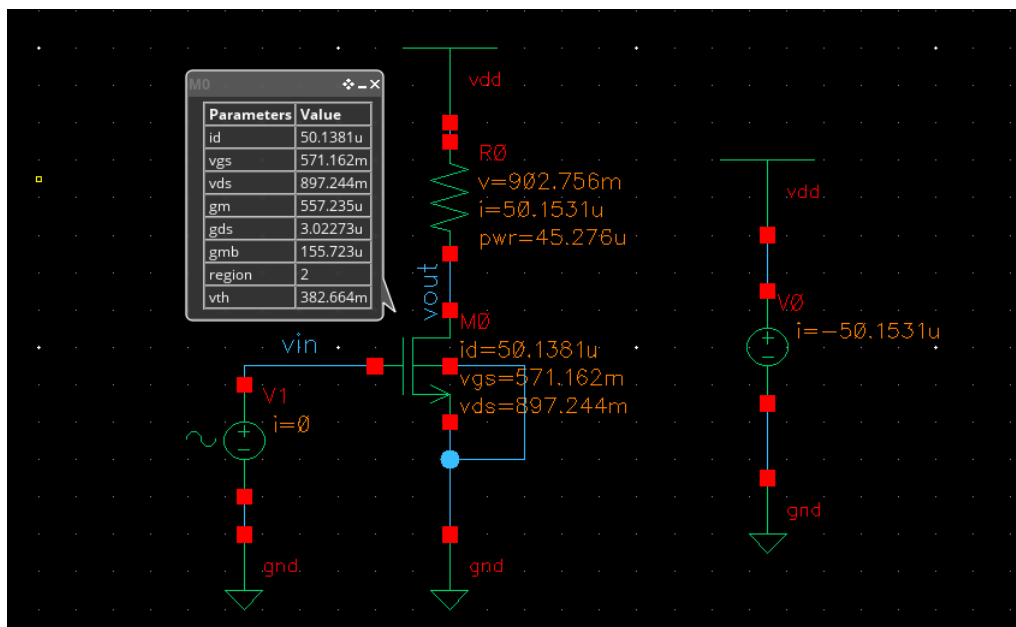


Fig.5 CS schematic with OP parameters simulation

OP parameter	Part 1 Result	CS Simulation Result
$I_{DQ}$	50uA	50.1381uA
$g_m$	555.39uS	557.235uS
$g_{ds}$	3.014uS	3.02273uS
$r_o$	331.785k $\Omega$	330.827k $\Omega$
$V_{gsQ}$	571.1623mV	571.1623mV

And as shown in previous table that there is a great agreement between our results in part 1 and CS amplifier simulation part.

And as shown in figure that region of MOSFET equal 2 which mean that MOSFET is in saturation region.

- $R_D$  vs  $r_o$ :

As shown from fig.6 that

$r_o = 330.8k\Omega$ , and we have value of  $R_D = 18k\Omega$ . So  $r_o \gg R_D$ , therefor we can neglect the value of  $r_o$  as the two resistances are connected in parallel.

And this is clear also in fig.6 simulation results of CS amplifier that

$$R_{out} = 17.9k\Omega \approx R_D.$$

If we use minimum channel length we

have to take the value of  $r_o$  in consideration because its value will decrease following the relation  $r_o = \frac{1}{\lambda I_{DS}} \rightarrow \lambda \propto \frac{1}{L} \rightarrow \therefore r_o \propto L$ .

1	
W	27.35E-6
M0:id	50.14E-6
M0:gm	557.2E-6
M0:gds	3.023E-6
M0:gmb	155.7E-6
M0:vgs (V)	571.2E-3
M0:region	2
M0:ron	17.90E3
M0:rout	330.8E3

Fig.6 OP parameters from CS amplifier simulation

- Intrinsic gain of MOSFET will be:

$$A_v = g_m * r_o = 557.2\mu S * 330.8k\Omega = 184.3217.$$

- Amplifier gain analytically:

$$A_v = g_m * (R_D \parallel r_o) = 9.5.$$

And from previous calculations it's clear that intrinsic gain is much greater than amplifier gain.

- AC Analysis:

$$\text{Amplifier gain magnitude } A_v = \frac{V_{out}}{V_{in}} = 9.5.$$

$$\text{Amplifier gain in dB } A_v = 20 * \log\left(\frac{V_{out}}{V_{in}}\right) = 19.55.$$

And we select value of input voltage to be 1 volt and plot output voltage which is considered to be voltage gain as shown in fig.7, and this meet our spec.

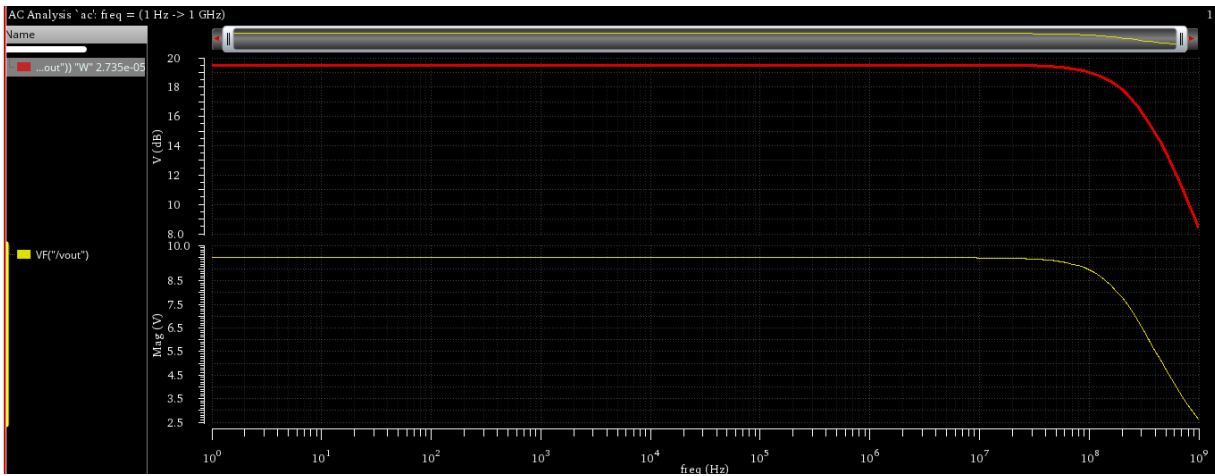


Fig.7 AC analysis simulation result for CS amplifier

## 2. Gain Non-Linearity:

- Output voltage  $V_{out}$  versus input voltage  $V_{gs}$ :

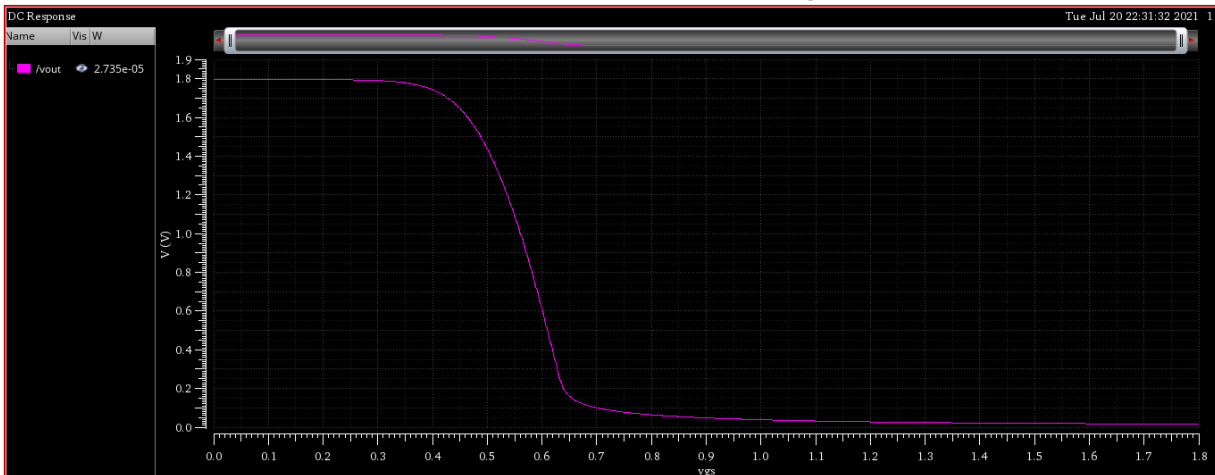


Fig.8 Vout versus Vin

As shown in fig.8 that the relation between  $V_{out}$  and  $V_{in}$  which is the gain relation is a non-linear relation and this because of dependance of gain on  $g_m$ , as the gain equation as following  $A_v = g_m * R_D$ , and  $g_m$  is a strong dependant on input voltage  $V_{gs}$ .

- Derivative of  $V_{out}$  versus  $V_{in}$ :

As shown in fig.9 that derivative of  $V_{out}$  is not constant value and this because that relation between  $V_{out}$  and  $V_{in}$  is not a linear relation due to dependance on  $g_m$  which is dependent on input voltage  $V_{gs}$ .

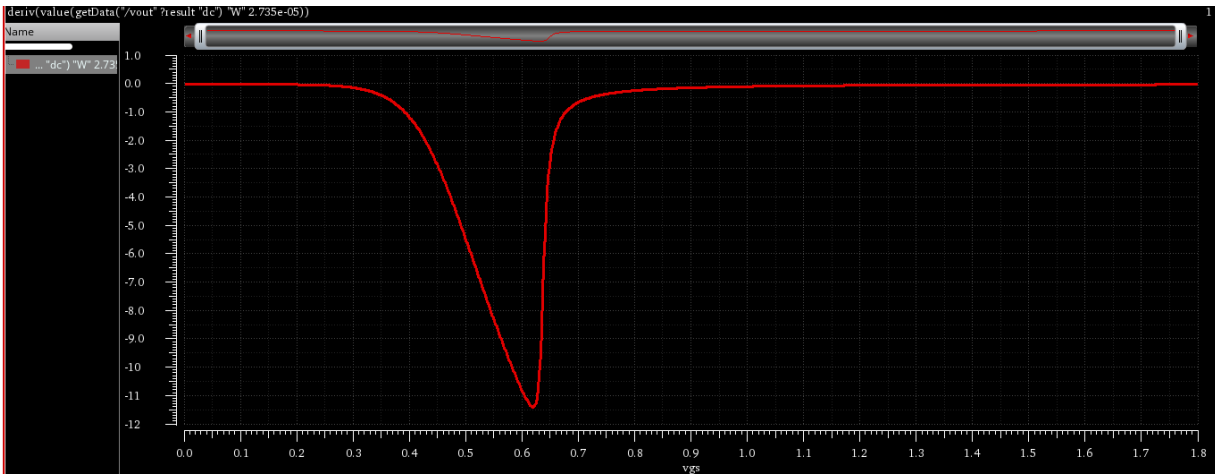


Fig.9 derivative of Vout versus Vin

- Transient analysis by a sine wave superimposed on input DC voltage level:

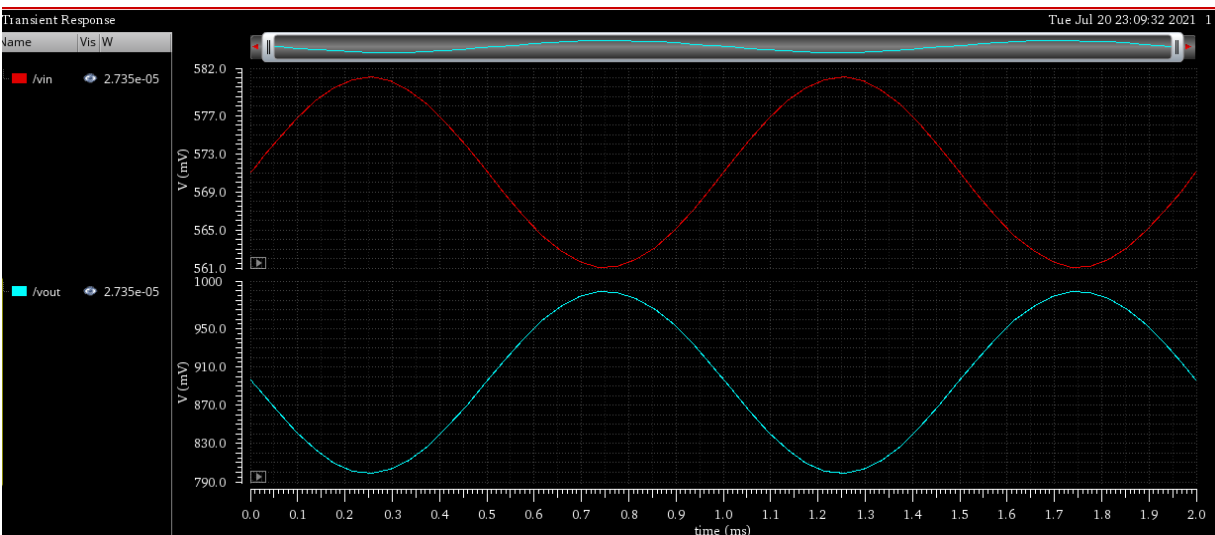


Fig.10 transient analysis simulation for input voltage and output voltage

- $g_m$  versus time simulation:  
As shown in fig.11 that  $g_m$  is varied with time and this proves the dependence of  $g_m$  on input voltage  $V_{gs}$  which also depend on time, so  $g_m$  is strong dependent on input voltage  $V_{gs}$ .

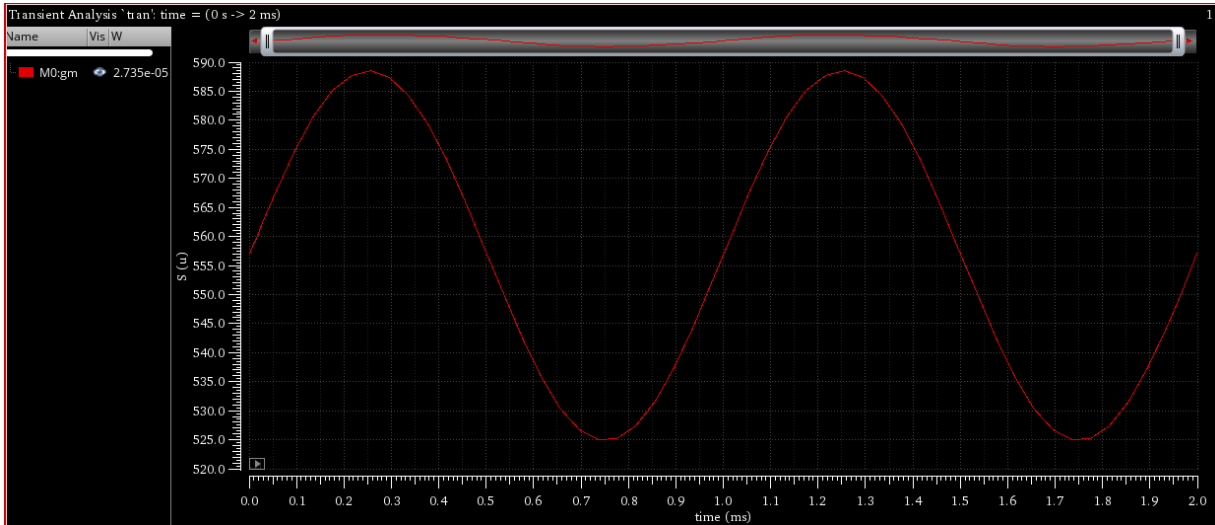


Fig.11  $g_m$  versus time in transient analysis

- From previous analysis it's clear that our amplifier is a non-linear amplifier because the relation between it's input voltage and output voltage is a non-linear relation, this because the gain of amplifier is dependant on  $g_m$  which is strongly dependant on input voltage  $V_{gs}$ , and this cause the non-linearity in the amplifier gain.