


# Lab 06

## Differential Amplifier

### Part 1: Sizing Chart


- Given Parameters in this Lab:

|                          |      |
|--------------------------|------|
| MOSFET Length L          | 1um  |
| Supply Voltage $V_{ds}$  | 1.8V |
| Tail Current $I_{ss}$    | 40uA |
| Differential Gain        | 8    |
| Common Mode Output Level | 0.7  |

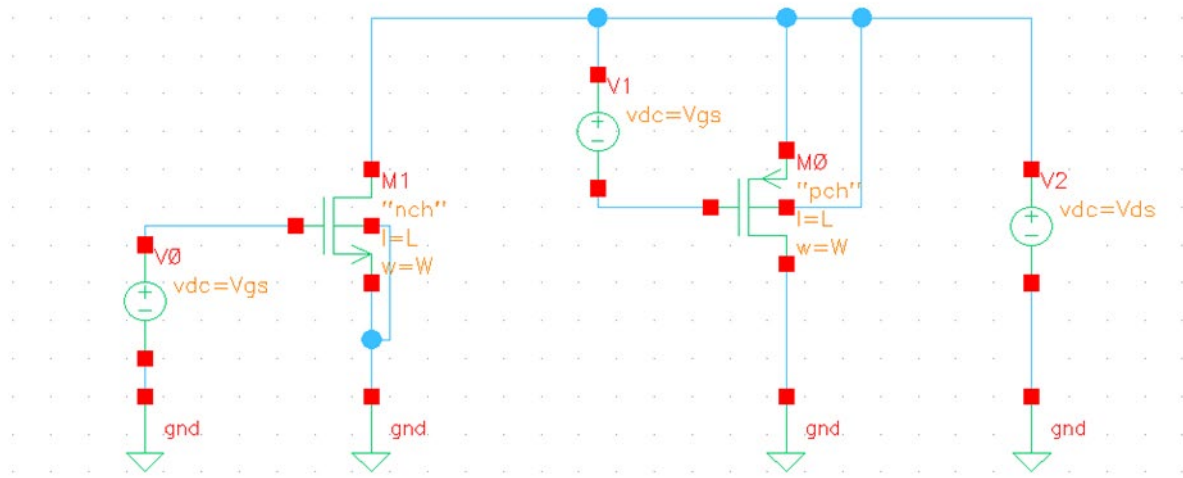


Schematic used in sizing
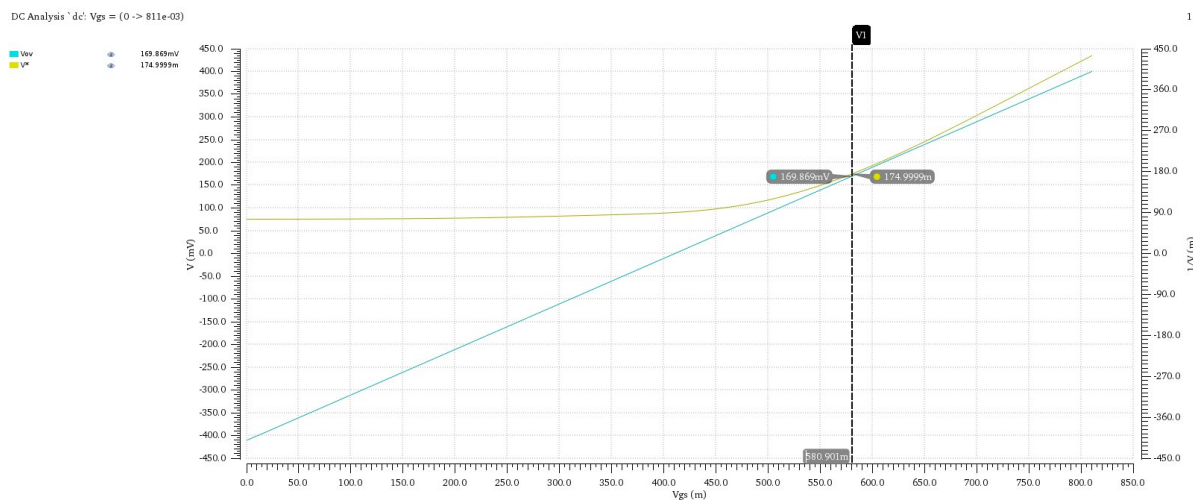
$$\text{As } A_V = \frac{2 \cdot V_{RD}}{V^*} \rightarrow V^* = \frac{2 \cdot V_{RD}}{A_V} = 0.175v.$$



$V_{ov}$  &  $V^*$  versus  $V_{gs}$  sweep

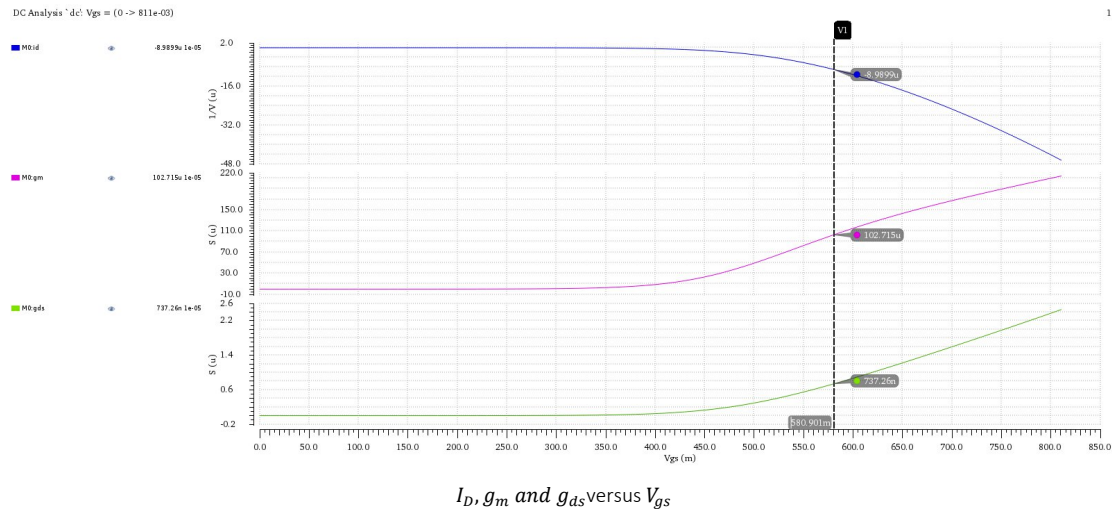From previous graphs we find at  $V_Q^* = 175mV \rightarrow V_{gsQ} = 580.901mV$  and  $V_{ovQ} = 169.896mV$ .




From previous graph at  $V_{gs} = 580.901mV$ , we have  $I_{dX} = 8.9899uA$ ,  $g_{mX} = 102.715uS$  and  $g_{dsX} = 737.26nS$ .


Using cross multiplication as  $I_d \propto W$ , we find that  $W=11.126um$ .

Also  $g_m = 114.28uS$ , and  $g_{ds} = 820.275nS$  @  $W=11.126um$ .

## Part 2: Differential Amplifier

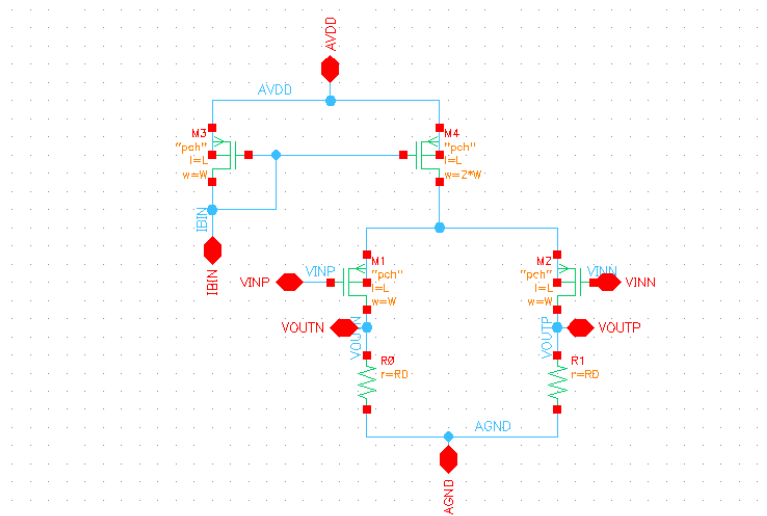

Differential pair schematic

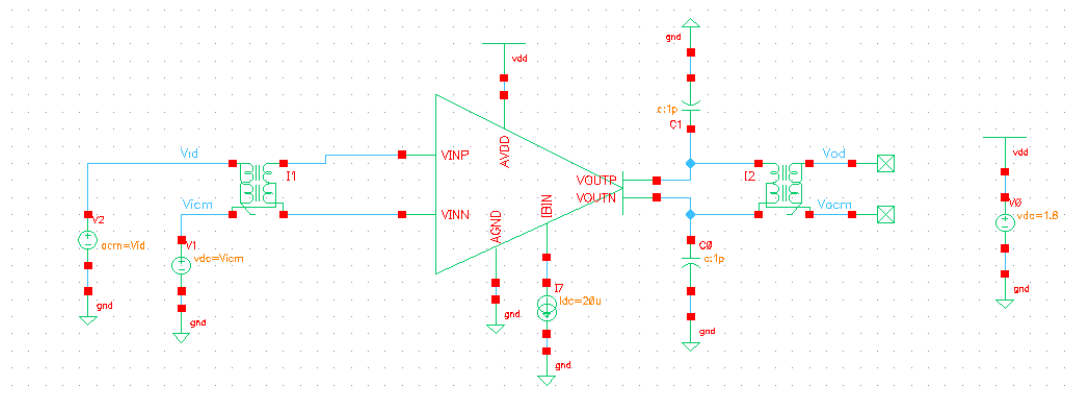

Differential pair symbol + testbench


- Input Common Mode Calculations:

$$V_{icmMAX} = -V_{gs} - V^* + V_{dd} = -580.901m - 175m + 1.8 = 1.044 V$$

$$V_{icmMIN} = -V_{th} + V_{RD} = -411m + 0.7 = 0.289 V$$

$$V_{icm} = \frac{V_{icmMAX} + V_{icmMIN}}{2} = 0.664 V$$


## 1) OP Simulation:

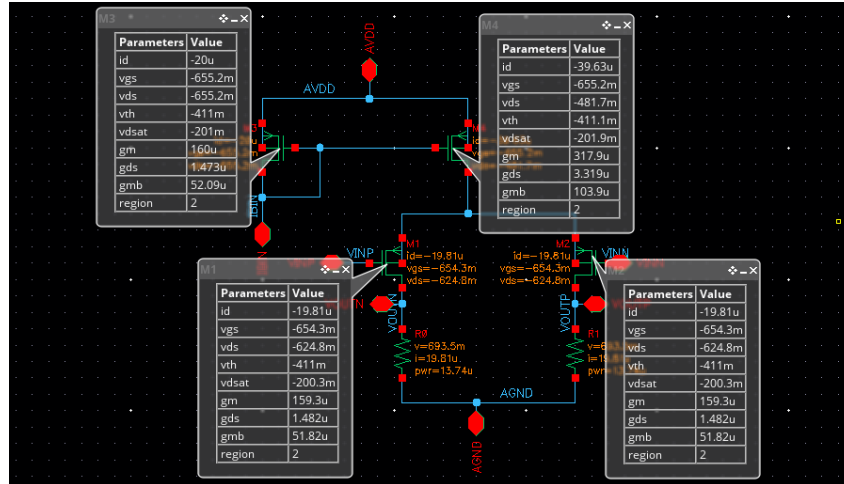

Op analysis results from cadence simulation

As shown that all MOSFET's regions equal 2 which mean that all transistors in saturation.

## 2) Diff Small Signal css:

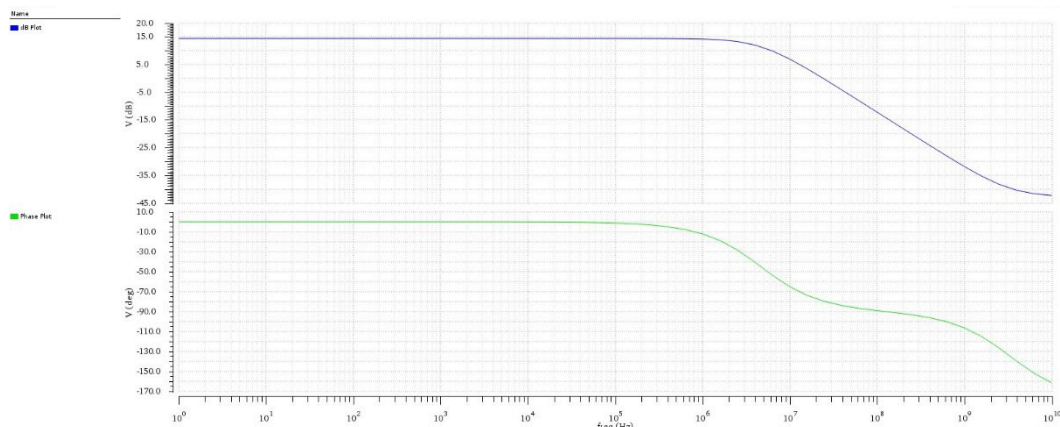

Bode plot of small signal differential gain

| Test                            | Output     | Nominal | Spec | Weight | Pass/Fail |
|---------------------------------|------------|---------|------|--------|-----------|
| TrainLAB:lab06_Diff_testbench:1 | Mag Plot   |         |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | Gain Mag   | 5.299   |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | Phase Plot |         |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | Gain dB    | 14.48   |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | BW         | 4.763M  |      |        |           |

DC gain and bandwidth from simulation results


- Analytical Results:

$$V_{RD} = I_D * R_D \rightarrow R_D = \frac{V_{RD}}{I_D} = \frac{0.7}{20u} = 35k\Omega$$

$$|A_V| = g_m * R_D = 159.3u * 35k = 5.5755$$

$$BW = \frac{1}{2\pi * RD * CL} = 4.547MHz$$

### 3) CM Small Signal css:

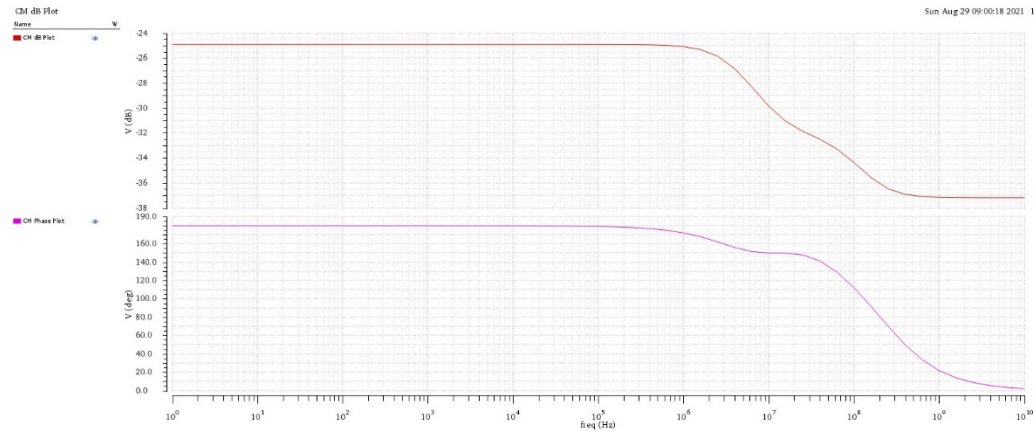

Bode plot of CM small signal gain

| Test                            | Output        | Nominal | Spec | Weight | Pass/Fail |
|---------------------------------|---------------|---------|------|--------|-----------|
| TrainLAB:lab06_Diff_testbench:1 | CM Gain       | 56.93m  |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | CM Gain dB    | -24.89  |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | CM BW         | 5.764M  |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | CM dB Plot    |         |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | CM Phase Plot |         |      |        |           |
| TrainLAB:lab06_Diff_testbench:1 | CM Mag Plot   |         |      |        |           |


DC gain and bandwidth from simulation results

- Analytical Results:

$$|A_V| = \frac{g_m * R_D}{1 + 2(g_m + g_{mb})R_{ss}} = 43.4m$$

CM small signal gain is less than 1 as the common mode is partially rejected, and not affect on the output due to degeneration by large resistance  $R_{ss}$ .

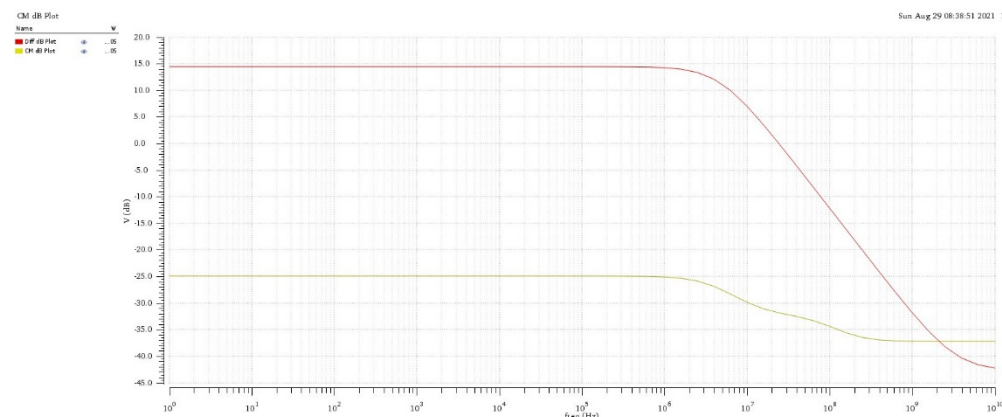- The variations in  $A_{vcm}$  at high frequency gain because tail current source is shunted by capacitance so at high frequency another pole due to this capacitance come to action which affects on bode plot and also impedance increases.



Avd & Avcm dB Plots


As shown simulation results will be 93.07

- Analytical Results:

$$CMRR = \frac{A_{vd}}{A_{vcm}} = 2(g_m + g_{mb})R_{ss} = 127.8$$

- Variation at high frequency due to capacitance which shunt  $R_{ss}$  and decrease impedance and come into action with pole.

#### 4) Diff Large Signal css:

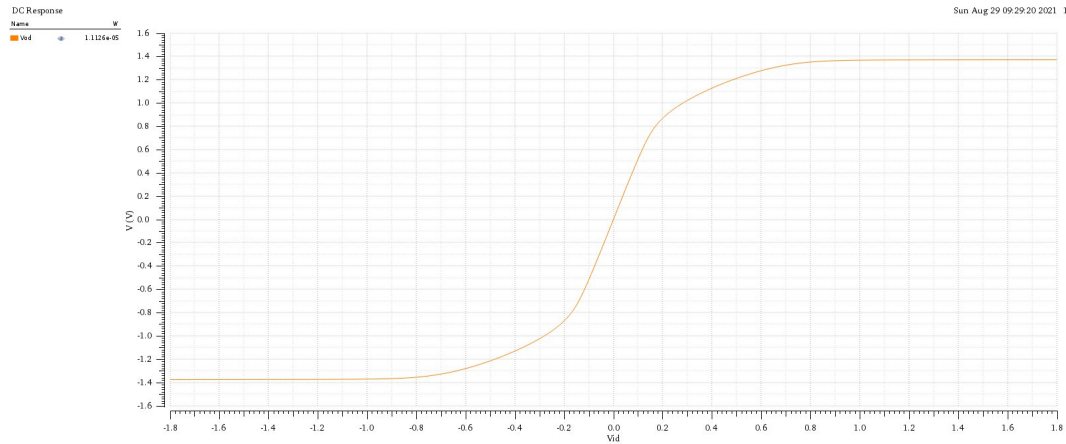


Vid versus sweep Vod

- Analytical solution for valid range:

$$-R_D * I_{SS} \rightarrow R_D * I_{SS} = -1.4 \rightarrow 1.4$$

#### 5) CM Larg Signal css:

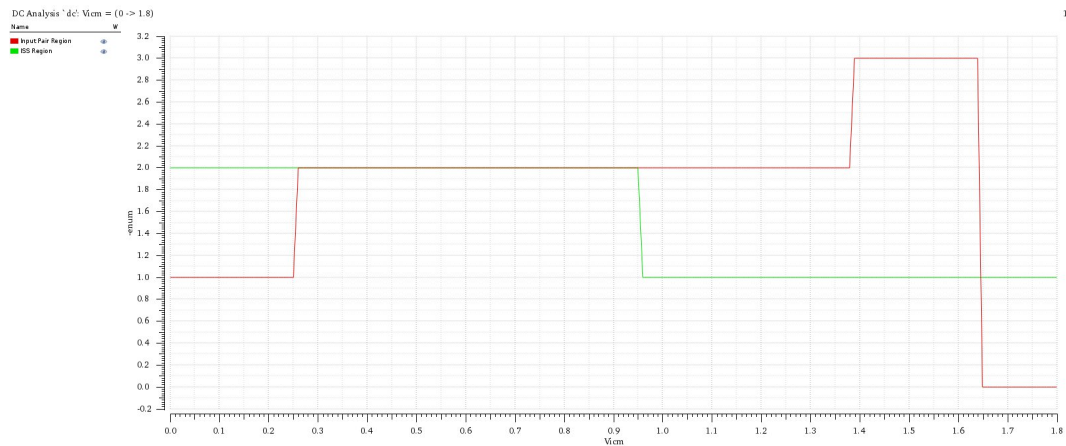


Region versus Vcm sweep

- Input common mode range from simulation as shown from 0.29 to 0.98 which meet with hand analysis results for CMIR


$$V_{icmMAX} = -V_{gs} - V^* + V_{dd} = -580.901m - 175m + 1.8 = 1.044 V$$

$$V_{icmMIN} = -V_{th} + V_{RD} = -411m + 0.7 = 0.289 V$$

#### 6) CM Larg Signal css:

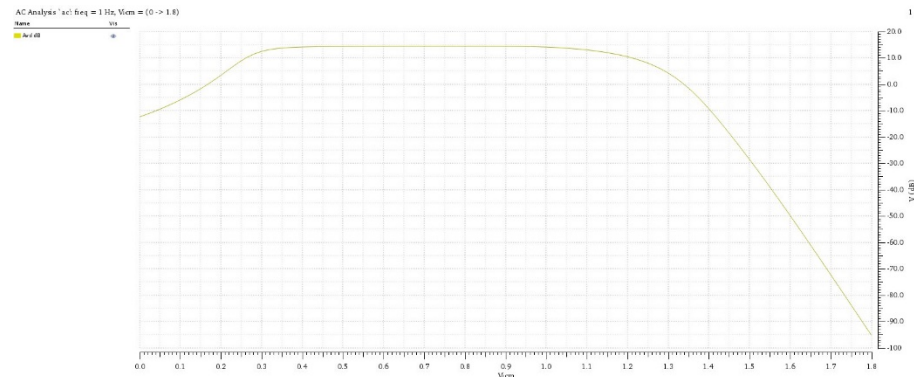

Vid versus Vicm sweep @ f=1Hz

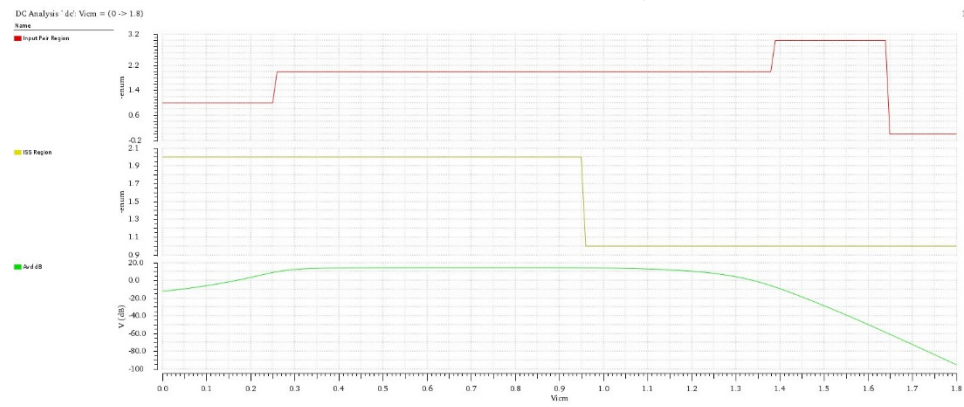

Regions and Vid versus CM at certain frequency